
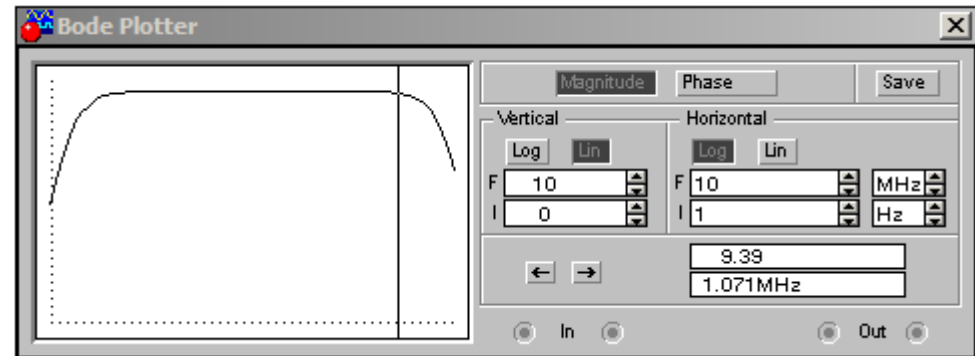


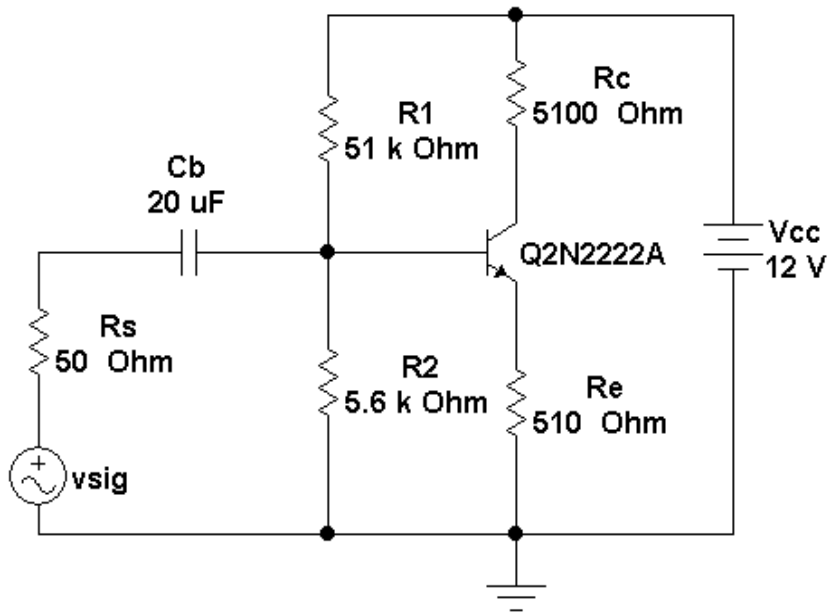

# *High Frequency BJT Model*

## *Gain of 10 Amplifier – Non-ideal Transistor*




Gain starts dropping at about 1MHz.


Why!

Because of internal transistor capacitances that we have ignored in our models.
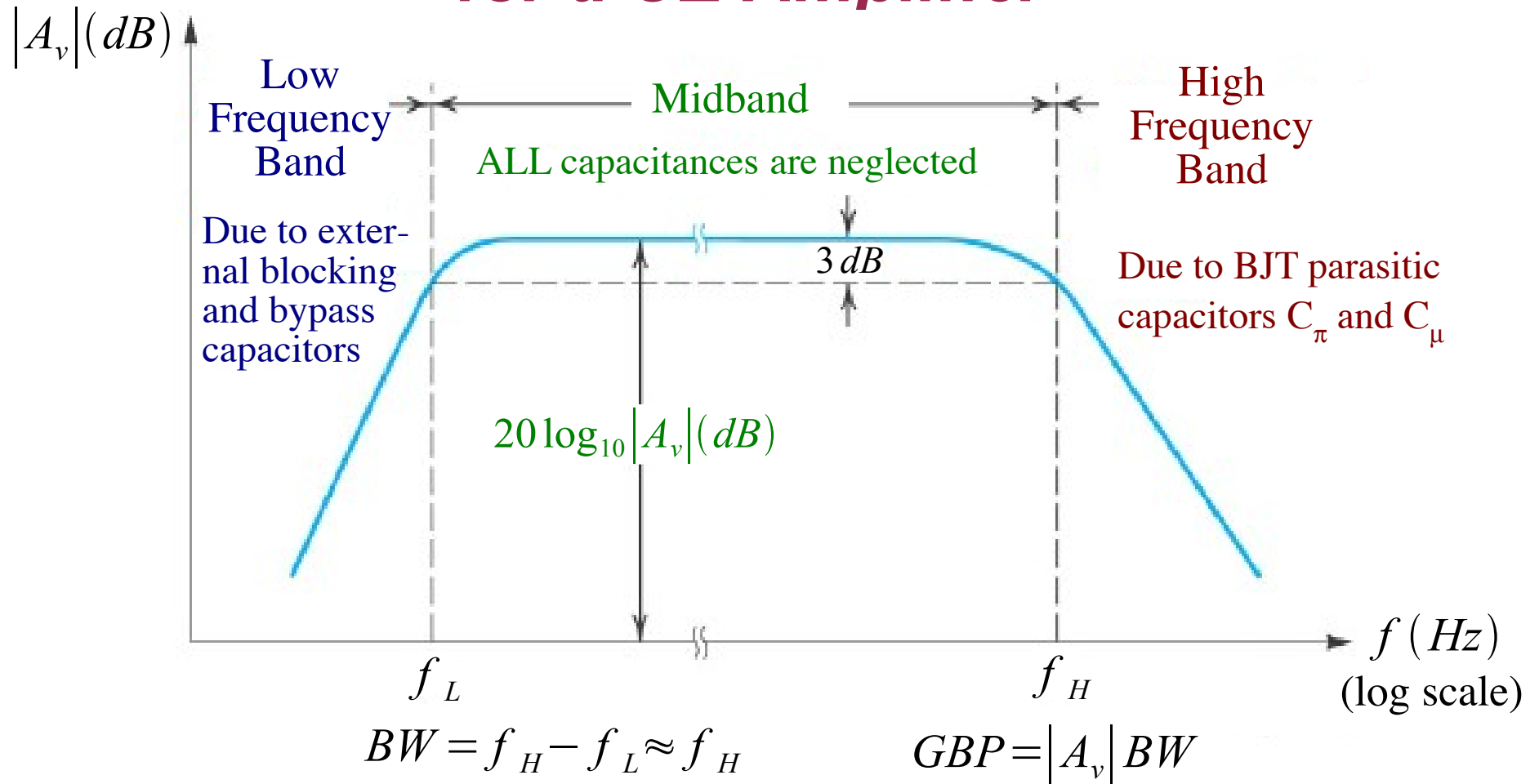
## *Sketch of Typical Voltage Gain Response for a CE Amplifier*



## High Frequency Small-signal Model

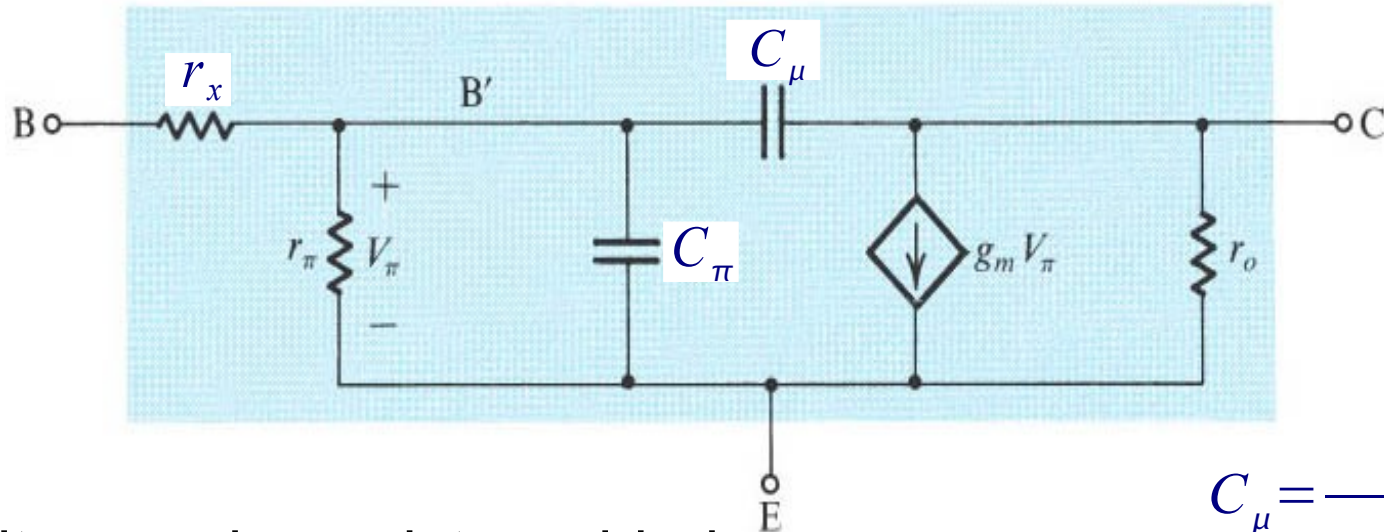

SPICE  
CJC =  $C_{\mu 0}$   
CJE =  $C_{je0}$   
TF =  $\tau_F$   
RB =  $r_x$

$$C_{\mu} = \frac{C_{\mu 0}}{\left(1 + \frac{V_{CB}}{V_{0c}}\right)^m}$$

$$C_{\pi} = C_{de} \frac{+C_{je0}}{\left(1 - \frac{V_{BE}}{V_{0e}}\right)^m} \approx C_{de} + 2C_{je0}$$

$C_{de} = \tau_F g_m$   
 $\tau_F$  = forward-base transit time

Two capacitors and a resistor added.  
A base to emitter capacitor,  $C_{\pi}$   
A base to collector capacitor,  $C_{\mu}$   
A resistor,  $r_x$ , representing the base terminal resistance ( $r_x \ll r_{\pi}$ )


## *High Frequency Small-signal Model*

The internal capacitors on the transistor have a strong effect on circuit high frequency performance! They attenuate base signals, decreasing  $v_{be}$  since their reactance approaches zero (short circuit) as frequency increases.

As we will see later  $C_\mu$  is the principal cause of this gain loss at high frequencies. At the base  $C_\mu$  looks like a capacitor of value  $k C_\mu$  connected between base and emitter, where  $k > 1$  and may be  $\gg 1$ .

This phenomenon is called the *Miller Effect*.

## Frequency-dependent “beta” $h_{fe}$

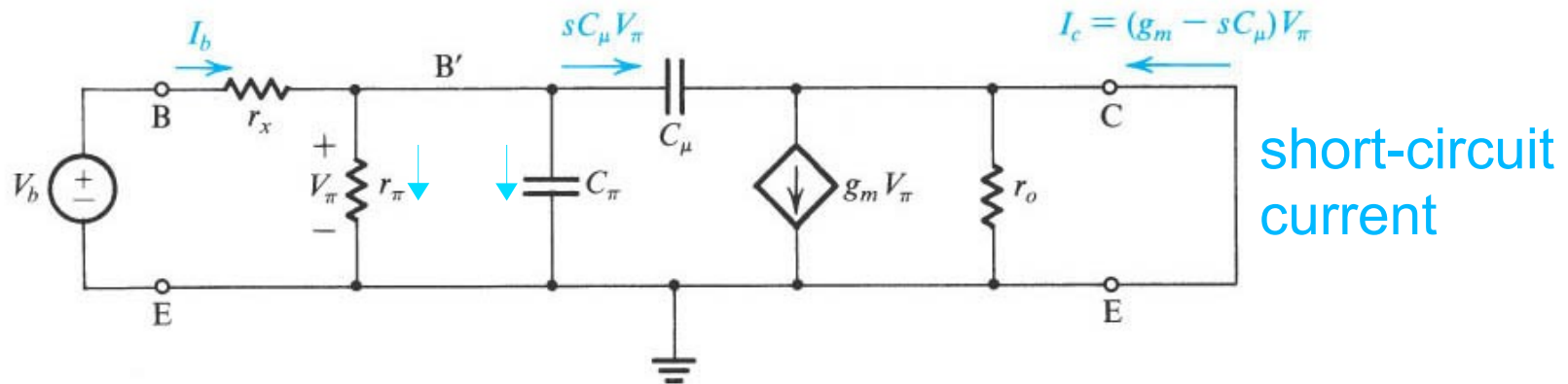


The relationship  $i_c = \beta i_b$  does not apply at high frequencies  $f > f_H$ !

Using the relationship  $-i_c = f(V_{\pi})$  – find the new relationship between  $i_b$  and  $i_c$ . For  $i_b$  (using *phasor notation* ( $I_x$  &  $V_x$ ) *for frequency domain analysis*):

@ node B': 
$$I_b = \left( \frac{1}{r_{\pi}} + sC_{\pi} + sC_{\mu} \right) V_{\pi} \quad \text{where } r_x \approx 0 \quad (\text{ignore } r_x)$$

**NOTE:**  $s = \sigma + j\omega$ , in sinusoidal steady-state  $s = j\omega$ .
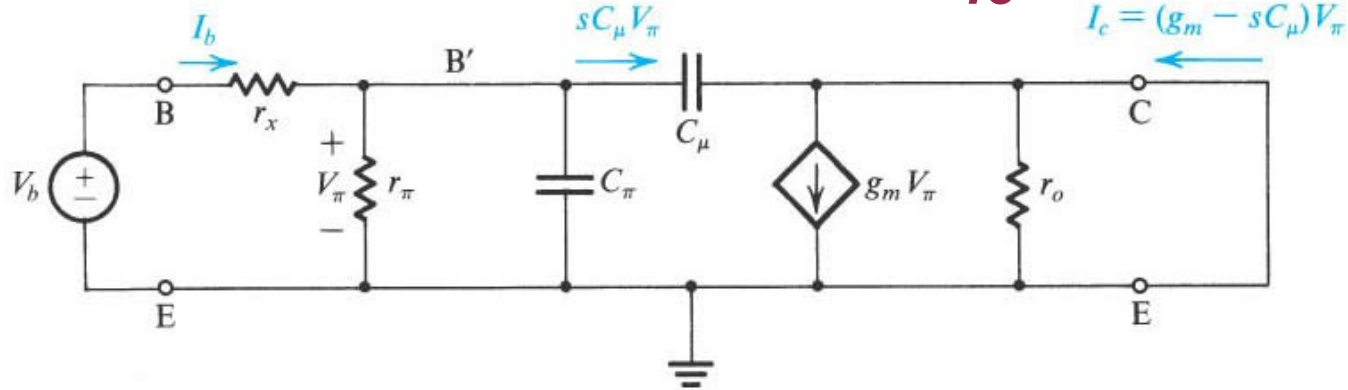
## Frequency-dependent $h_{fe}$ or “beta”



$$I_b = \left( \frac{1}{r_\pi} + s C_\pi + s C_\mu \right) V_\pi \quad @ \text{ node C: } I_c = (g_m - s C_\mu) V_\pi \quad (\text{ignore } r_o)$$

Leads to a new relationship between the  $I_b$  and  $I_c$ :

$$h_{fe} = \frac{I_c}{I_b} = \frac{g_m - s C_\mu}{\frac{1}{r_\pi} + s C_\pi + s C_\mu}$$

## Frequency Response of $h_{fe}$

$$h_{fe} = \frac{g_m - s C_\mu}{\frac{1}{r_\pi} + s C_\pi + s C_\mu}$$

multiply N&D by  $r_\pi$  and set  $s = j\omega$

$$h_{fe} = \frac{(g_m - j\omega C_\mu) r_\pi}{1 + j\omega (C_\pi + C_\mu) r_\pi}$$

factor N to isolate  $g_m$

$$h_{fe} = \frac{(1 - j\omega \frac{C_\mu}{g_m}) \underbrace{g_m r_\pi}_\beta}{1 + j\omega (C_\pi + C_\mu) r_\pi}$$

$$g_m = \frac{I_C}{V_T} \quad r_\pi = \beta \frac{V_T}{I_C}$$

For small  $\omega = \omega_{low}$ :  $\omega_{low} \frac{C_\mu}{g_m} \ll 1 < \frac{1}{10}$

and:  $\omega_{low} (C_\pi + C_\mu) r_\pi \ll 1 < \frac{1}{10}$

**Note:**  $\omega_{low} (C_\pi + C_\mu) r_\pi = \omega_{low} (C_\pi + C_\mu) \frac{\beta}{g_m} \gg \omega_{low} \frac{C_\mu}{g_m}$

We have:


$$h_{fe} = g_m r_\pi = \beta$$



## Frequency Response of $h_{fe}$ cont.

$$h_{fe} = \frac{(1 - j\omega \frac{C_\mu}{g_m}) g_m r_\pi}{1 + j\omega (C_\pi + C_\mu) r_\pi} = \frac{\left(1 - j\frac{\omega}{\omega_z}\right)}{\left(1 + j\frac{\omega}{\omega_\beta}\right)} g_m r_\pi = \frac{\left(1 - j\frac{f}{f_z}\right)}{\left(1 + j\frac{f}{f_\beta}\right)} \beta$$

$\omega_\beta$

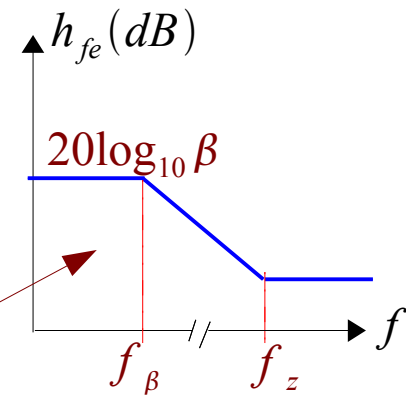

$$(C_\pi + C_\mu) r_\pi = (C_\pi + C_\mu) \frac{\beta}{g_m} \gg \frac{C_\mu}{g_m} \Rightarrow f_z \gg f_\beta$$

Hence, the lower break frequency or  $-3dB$  frequency is  $f_\beta$

$$f_\beta = \frac{1}{2\pi (C_\pi + C_\mu) r_\pi} = \frac{g_m}{2\pi (C_\pi + C_\mu) \beta} \quad \text{the upper:} \quad f_z = \frac{1}{2\pi C_\mu / g_m} = \frac{g_m}{2\pi C_\mu}$$

$$\text{where } f_z > 10 f_\beta$$

## *Frequency Response of $h_{fe}$ cont.*

Using Bode plot concepts, for the range where:  $f < f_\beta$

$$h_{fe} = g_m r_\pi = \beta$$

For the range where:  $f_\beta < f < f_z$  s.t.  $|1 - j f / f_z| \approx 1$

We consider the frequency-dependent numerator term to be 1 and focus on the response of the denominator:

$$h_{fe} = \frac{g_m r_\pi}{\left(1 + j \frac{f}{f_\beta}\right)} = \frac{\beta}{\left(1 + j \frac{f}{f_\beta}\right)}$$

## *Frequency Response of $h_{fe}$ cont.*

Neglecting numerator term:

$$h_{fe} = \frac{g_m r_\pi}{\left(1 + j \frac{f}{f_\beta}\right)} = \frac{\beta}{\left(1 + j \frac{f}{f_\beta}\right)}$$

And for  $f / f_\beta \gg 1$  (but  $< f / f_z$ ):

$$|h_{fe}| \approx \frac{\beta}{\left(\frac{f}{f_\beta}\right)} = \beta \frac{f_\beta}{f}$$

Unity gain bandwidth:  $|h_{fe}| = 1 \Rightarrow \beta \frac{f_\beta}{f} \mid_{f=f_T} = 1 \Rightarrow f_T = \beta f_\beta$

$$f_T = \frac{\omega_T}{2\pi} = \beta f_\beta$$

BJT unity-gain frequency or GBP

## *Frequency Response of $h_{fe}$ cont.*

$$\beta = 100 \quad r_{\pi} = 2500 \, \Omega \quad C_{\pi} = 12 \, pF \quad C_{\mu} = 2 \, pF \quad g_m = 40 \cdot 10^{-3} \, S$$

$$\omega_{\beta} = \frac{1}{(C_{\pi} + C_{\mu}) r_{\pi}} = \frac{10^{12} \cdot 10^{-3}}{(12 + 2) \cdot 2.5} = 28.57 \cdot 10^6 \, rps$$

$$f_{\beta} = \frac{\omega_{\beta}}{2\pi} = \frac{28.57}{6.28} 10^6 \, Hz = 4.55 \, MHz \quad f_T = \beta f_{\beta} = 455 \, MHz$$


$$\omega_z = \frac{g_m}{C_{\mu}} = \frac{40 \cdot 10^{-3} \cdot 10^{12}}{2} \, Hz = 20 \cdot 10^9 \, rps$$

$$f_z = \frac{\omega_z}{2\pi} = 3.18 \cdot 10^9 \, Hz = 3180 \, MHz$$


## *Scilab $f_T$ Plot*

```
//fT Bode Plot
Beta=100;
KdB= 20*log10(Beta);
fz=3180;
fp=4.55;
f= 1:1:10000;
term1=KdB*sign(f); //Constant array of len(f)
term2=max(0,20*log10(f/fz)); //Zero for f < fz;
term3=min(0,-20*log10(f/fp)); //Zero for f < fp;
BodePlot=term1+term2+term3;
plot(f,BodePlot);
```

## $h_{fe}$ Bode Plot

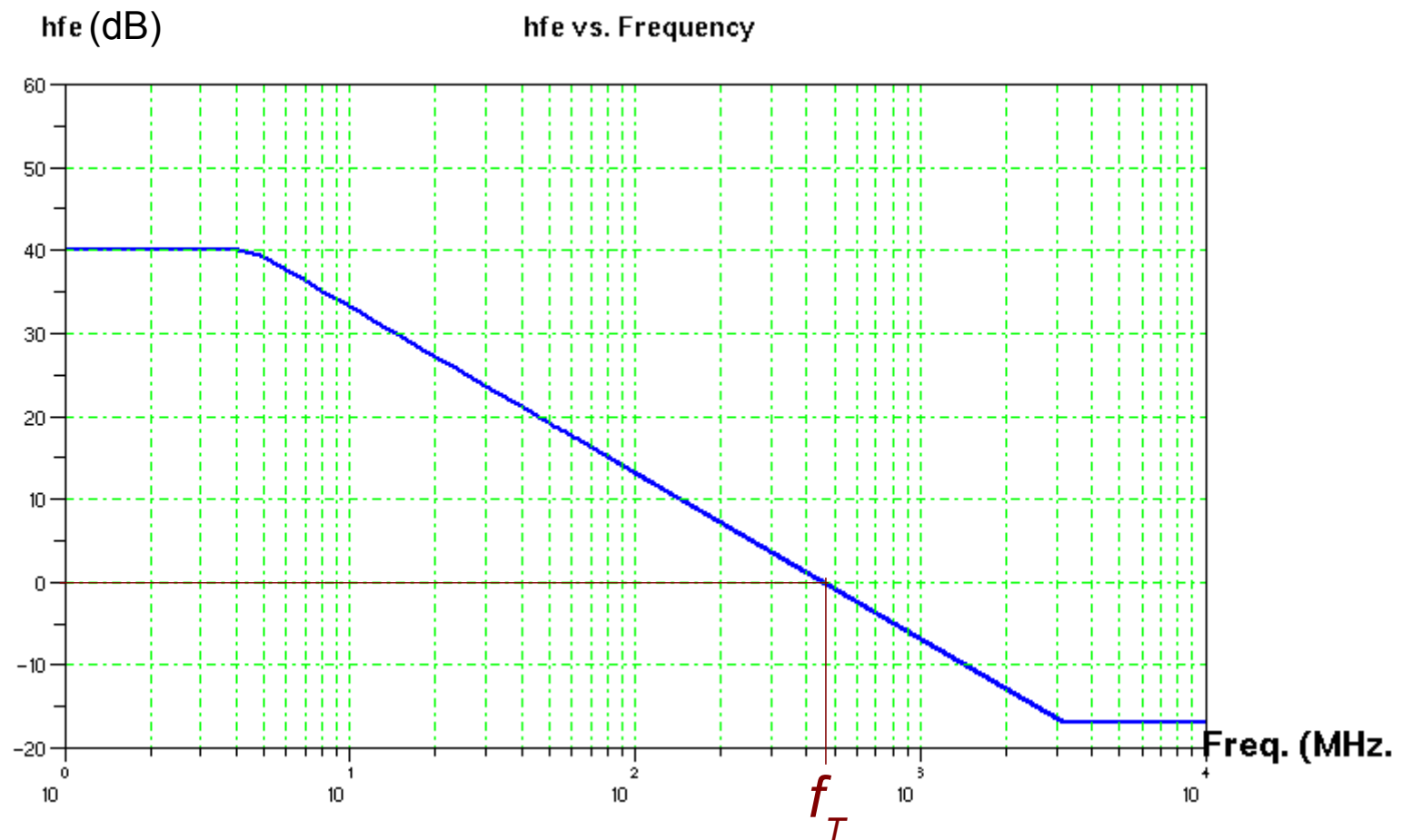


## Multisim Simulation

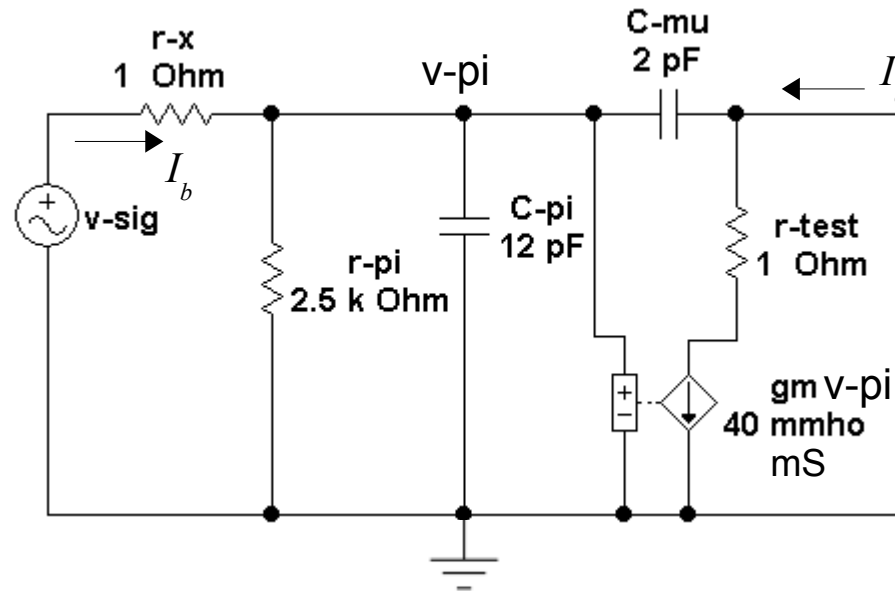

Insert 1 ohm resistors – we want to measure a current ratio.

$$h_{fe} = \frac{I_c}{I_b} = \frac{g_m - s C_\mu}{\frac{1}{r_\pi} + s(C_\pi + C_\mu)}$$


## Simulation Results

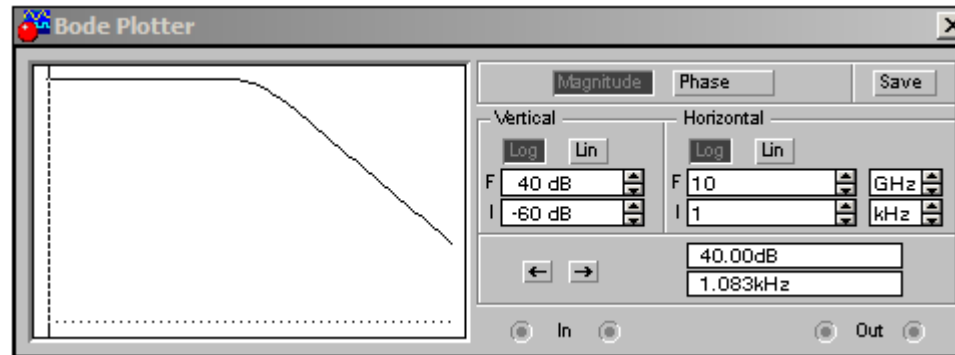

Low frequency  $|h_{fe}|$

Theory:
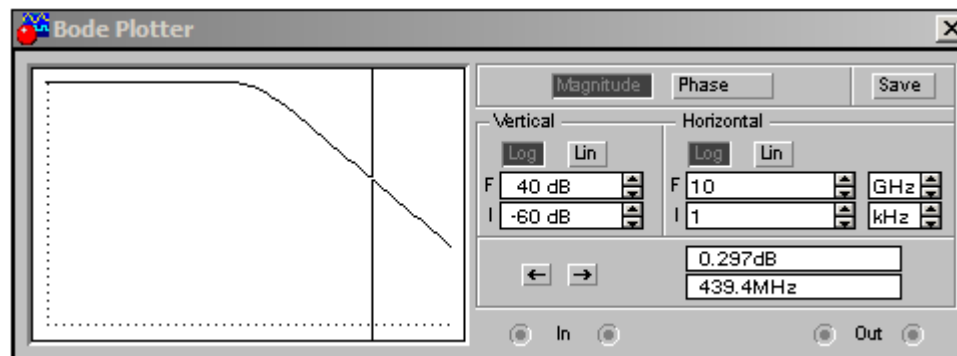
$$f_T = \beta f_\beta = 455 \text{ MHz}$$



Unity Gain frequency about **440 MHz**

