



**ISEN** | école  
d'ingénieurs  
LILLE

# **RF & MICROWAVE CIRCUITS**

**CIRCUITS RF & HYPER**

**2018-2019**

**AXEL FLAMENT**

**DAMIEN DUCATTEAU**

## REMINDER

$$\Gamma = \frac{Z - Z_0}{Z + Z_0}$$

Reflection coefficient is  
referenced to  $50\Omega$

If  $Z \rightarrow \Gamma$  then  $Z^* \rightarrow \Gamma^*$


$$Z = Z_0 \frac{1 + \Gamma}{1 - \Gamma}$$

$$a_2 = b_2 \Gamma_L$$

$$a_1 = b_1 \Gamma_S$$

## S-PARAMETERS

## REMINDER

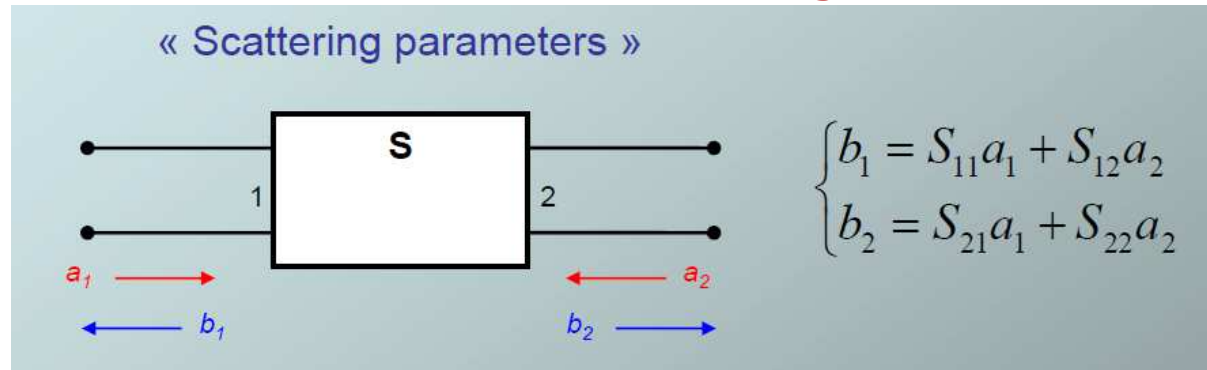

- $S_{11} = (b_1/a_1)_{a_2=0}$  = input reflection coefficient when the output is loaded by  $Z_0$
- $S_{12} = (b_1/a_2)_{a_1=0}$  = Reverse transmission coefficient when the input is loaded by  $Z_0$
- $S_{21} = (b_2/a_1)_{a_2=0}$  = Direct transmission coefficient when the output is loaded by  $Z_0$
- $S_{22} = (b_2/a_2)_{a_1=0}$  = output reflection coefficient when the input is loaded by  $Z_0$

## REMINDER-S parameters calculation


- To calculate the S-parameters matrix of a (passive) quadripole, it is more convenient to work with known elements (voltage and currents) rather than with incident and reflected power waves...
- 1<sup>st</sup> step : write equations with input and output currents and voltages
- 2<sup>nd</sup> step : Use the relationships :  $a_i + b_i = V_i / \sqrt{Z_0}$  and  $a_i - b_i = I_i \sqrt{Z_0}$
- 3<sup>rd</sup> step : Use the definitions of S parameters :  $S_{11} = (b_1 / a_1)_{a_2=0}$  for the 4 coefficients

**S-PARAMETERS**

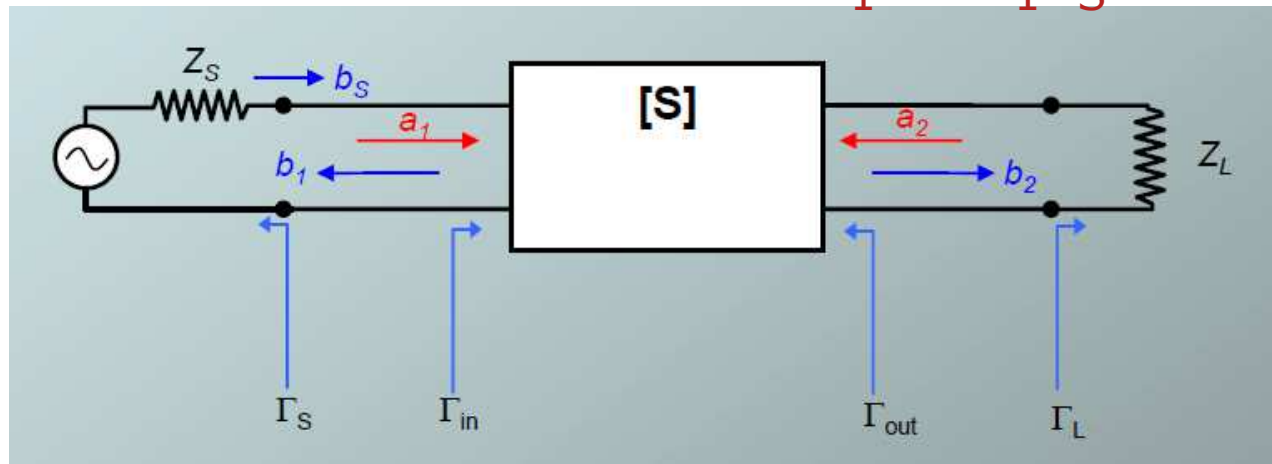**REMINDER**


$$\begin{cases} b_1 = S_{11}a_1 + S_{12}a_2 \\ b_2 = S_{21}a_1 + S_{22}a_2 \end{cases}$$

$$\begin{aligned} a_2 &= b_2 \Gamma_L \\ a_1 &= b_1 \Gamma_S \end{aligned}$$



- $\Gamma_{in} = b_1/a_1 = S_{11} + S_{12} a_2/a_1 = S_{11} + S_{12} \Gamma_L b_2/a_1$
- $\Gamma_{in} = S_{11} + S_{12} S_{21} \Gamma_L / (1 - S_{22} \Gamma_L)$
- $\Gamma_{out} = b_2/a_2 = S_{22} + S_{21} a_1/a_2 = S_{22} + S_{21} \Gamma_S b_1/a_2$
- $\Gamma_{out} = S_{22} + S_{21} S_{12} \Gamma_S / (1 - S_{11} \Gamma_S)$


## REMINDER – Power in AC circuits

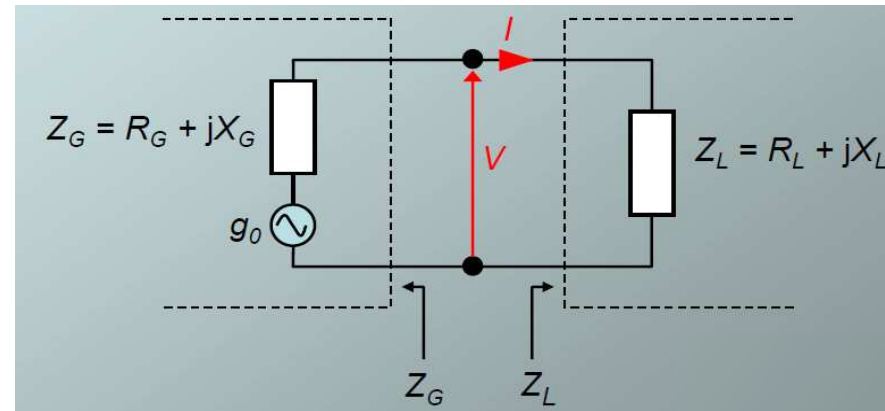

- Instantaneous power =  $v(t) \times i(t)$  [VA]
- Complex power =  $V \times I^*$  [VA], only for sinusoid signals
- Real or average power =  $\text{Re}(\text{complex power}) = \frac{1}{T} \int_{t_0}^{t_0+T} u(t)i(t)dt$  [W]
  - dissipated as heat
- Reactive power =  $\text{Im}(\text{complex power})$  [VAR]
  - No work
- Apparent power =  $|\text{complex power}|$  [VA]
- Power factor =  $\cos\Phi = \text{real power}/\text{apparent power}$  (ideally close to 1)

## IMPEDANCE MATCHING

### REMINDER

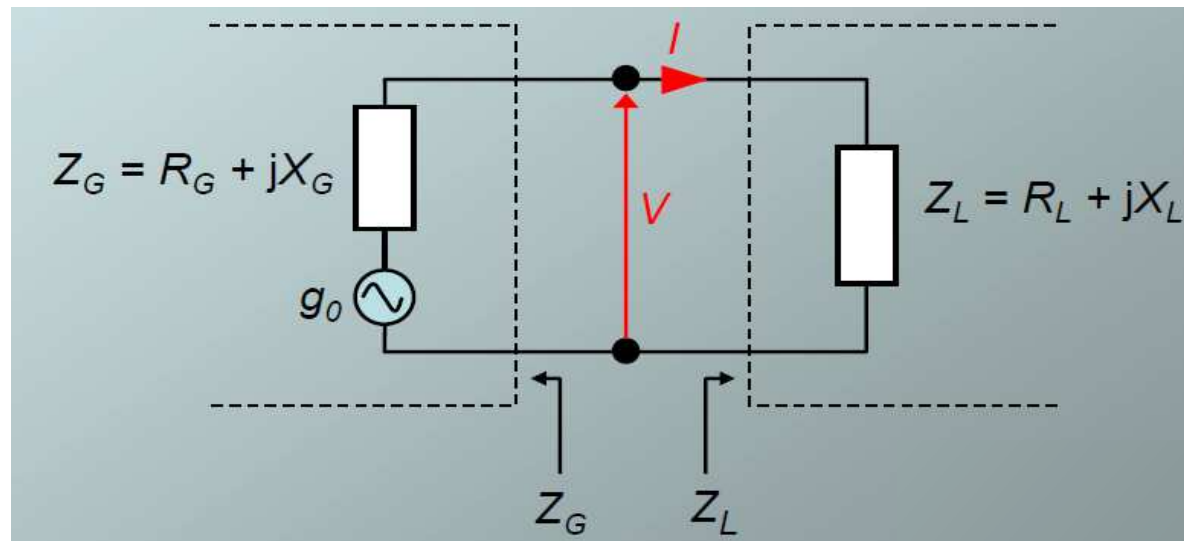

- Maximizing power transfer ?
- $P = 0.5 \operatorname{Re}(VI^*)$  maximized if  $Z_L = Z_G^*$
- In this case, the load receives all the available power from the source and delivered power to the load is maximized


## OUTLINE

- Transducic power gain and gain definitions
- $G_T$  calculation / Maximizing  $G_T$
- Unilaterality
- Stability
- Noise
- Methodology




POWER TRANSDUCIC GAIN

## Power transducic gain

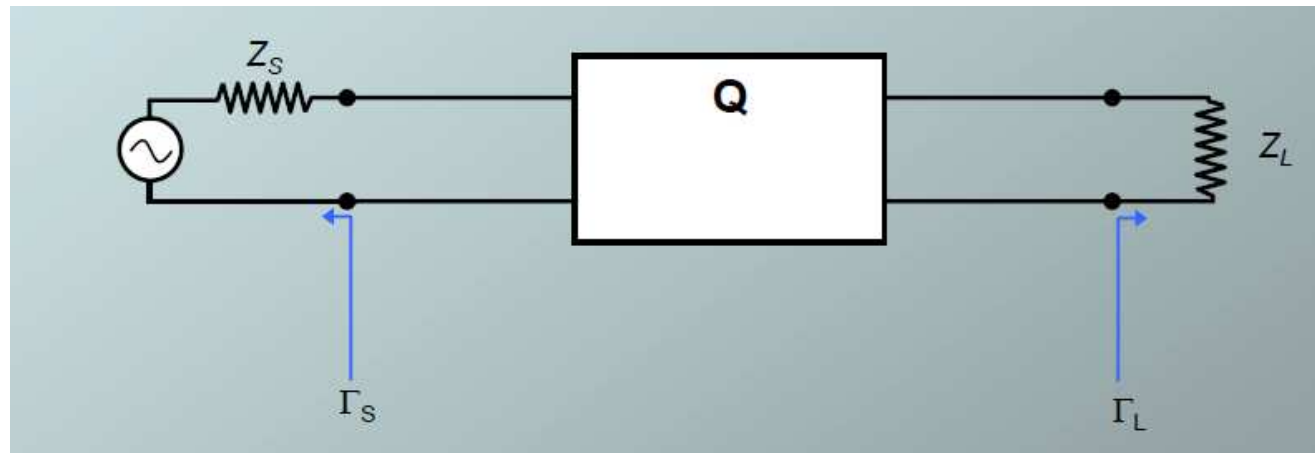


- Power Transducic Gain =  $G_T$  = Power delivered to the load/power available at the source

## Other gain definitions

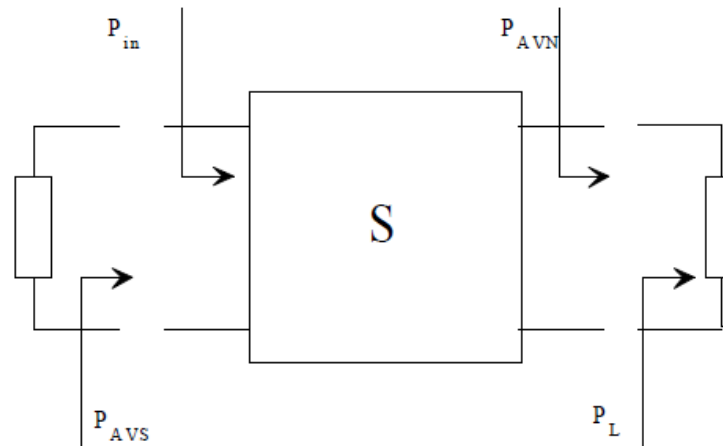

- $G_T = P_L / P_{AVs}$  = transducic gain = power delivered to the load / power available at the source
- $G_P = P_L / P_{in}$  = power gain = power delivered to the load / power at the input of the quadripole
- $G_A = P_{AVN} / P_{AVs}$  = available gain = power available at the output of the quadripole / power available at the source


## Other gain definitions

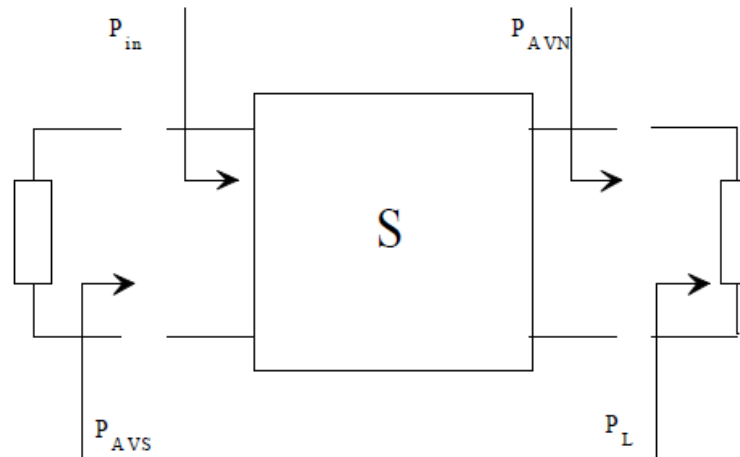

- $G_T \leq G_p$
- $G_T = G_p$  when the input is matched
- $G_T \leq G_A$
- $G_T = G_A$  when the output is matched

**POWER TRANSDUCIC GAIN**



**Power delivered to the load**

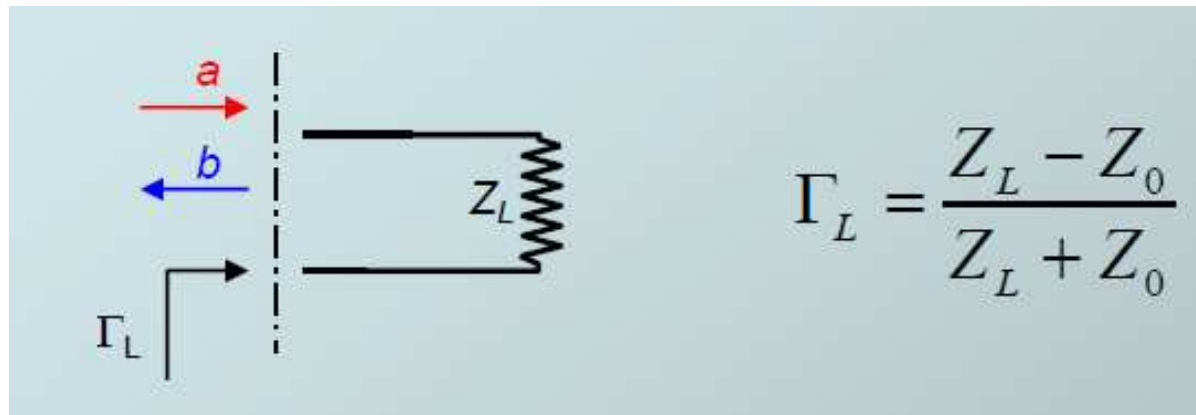

- Delivered Power = Incident Power – Reflected Power
- $= |a|^2 - |b|^2 = |a|^2 - |\Gamma_L|^2 |a|^2 = |a|^2 (1 - |\Gamma_L|^2)$

## POWER TRANSDUCIC GAIN


### Power available at the source

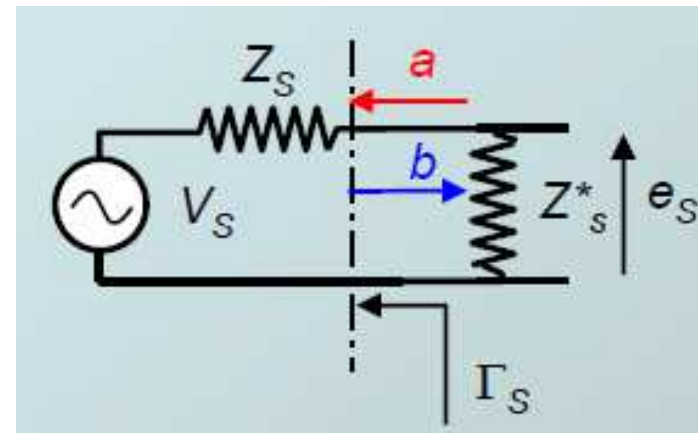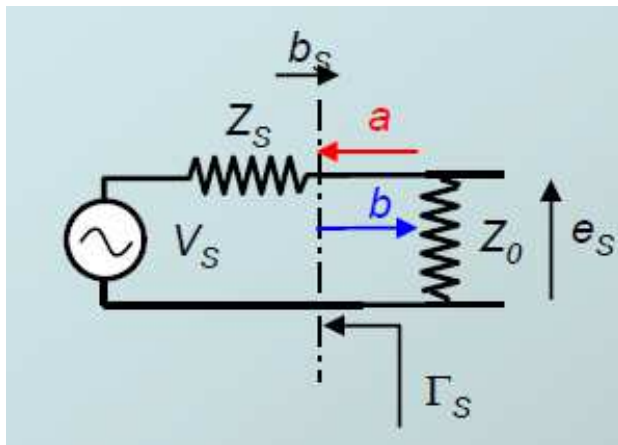

- Power available at the source = power delivered to the conjugate load
- $b = b_s + \Gamma_s a$
- $a = b \Gamma_s^*$
- So  $b = b_s / (1 - |\Gamma_s|^2)$
- $P_{avs} = |b|^2 - |a|^2 = |b_s|^2 / (1 - |\Gamma_s|^2)$


**POWER TRANSDUCIC GAIN**

**$G_T$  calculation**

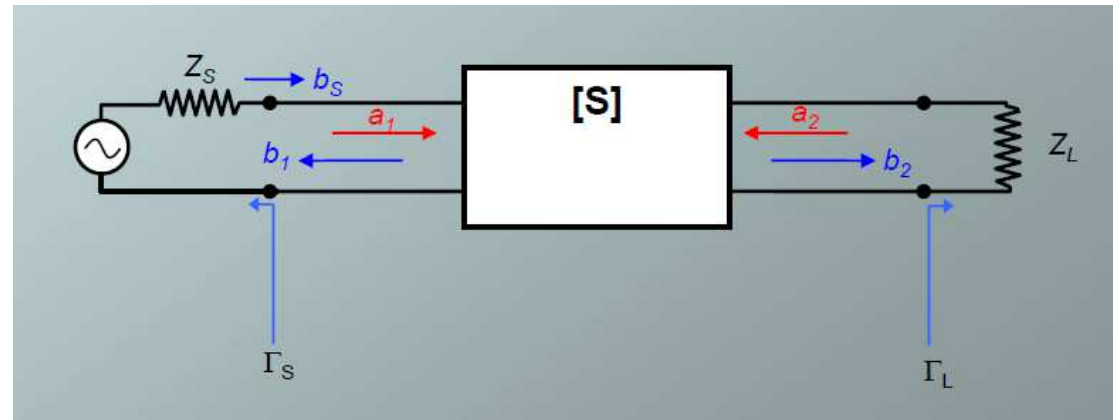


$$G_T = \frac{P_{del}}{P_{avs}} = \frac{|b_2|^2 (1 - |\Gamma_L|^2)}{|b_s|^2} = \frac{|b_2|^2}{|b_s|^2} (1 - |\Gamma_L|^2) (1 - |\Gamma_s|^2)$$

## $G_T$ calculation

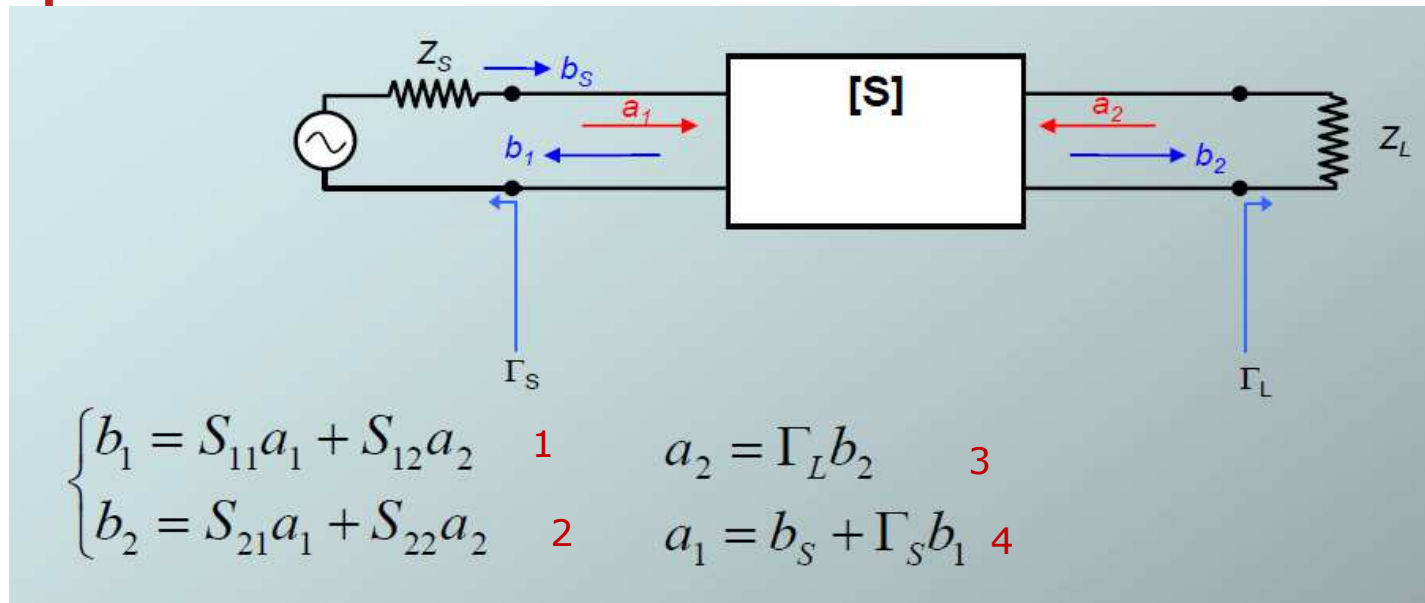

- (3) in (2) :  $b_2 = S_{21} a_1 / (1 - S_{22} \Gamma_L)$  (5)
- (1) in (4) :  $a_1 = b_s + \Gamma_S S_{11} a_1 + \Gamma_S S_{12} a_2 = b_s + \Gamma_S S_{11} a_1 + \Gamma_S S_{12} \Gamma_L b_2$
- So  $a_1 = (b_s + \Gamma_S S_{12} \Gamma_L b_2) / (1 - \Gamma_S S_{11})$
- In (5) ...


## $G_T$ calculation

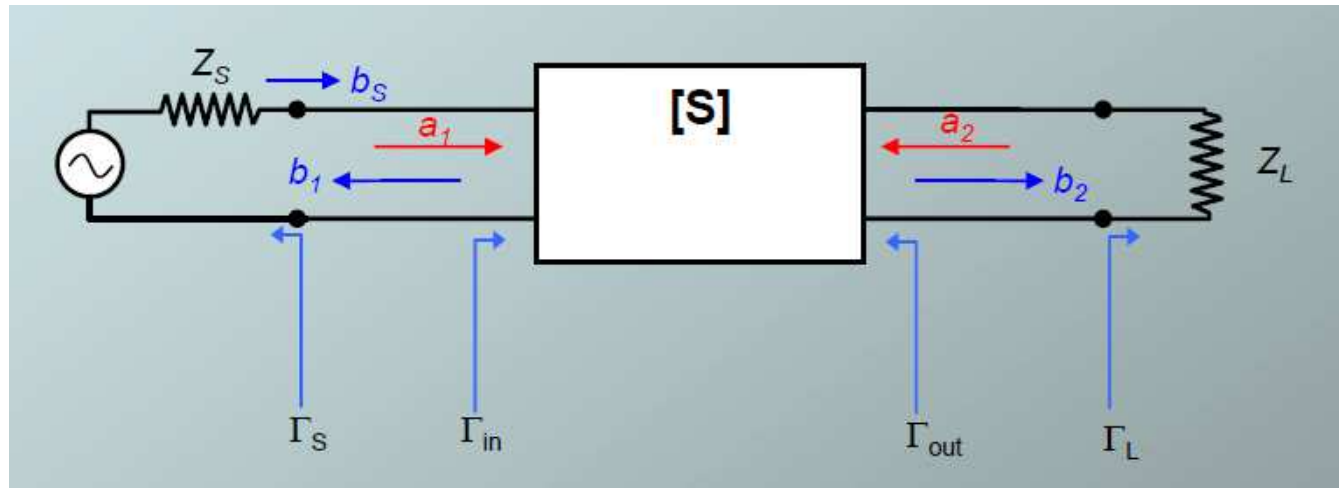

$$G_T = \frac{|S_{21}|^2 (1 - |\Gamma_S|^2) (1 - |\Gamma_L|^2)}{|(1 - S_{11}\Gamma_S)(1 - S_{22}\Gamma_L) - S_{21}S_{12}\Gamma_S\Gamma_L|^2}$$



## How to maximize $G_T$ ?

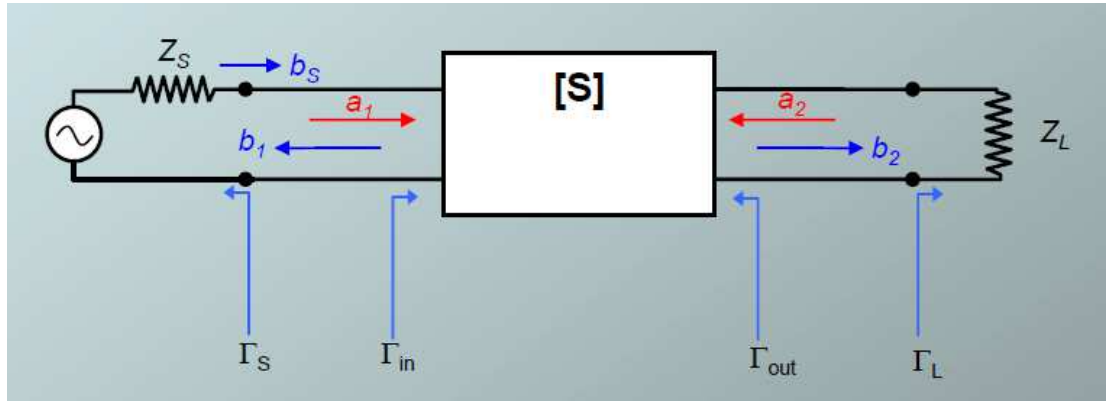

$$G_T = \frac{|S_{21}|^2 (1 - |\Gamma_S|^2) (1 - |\Gamma_L|^2)}{|(1 - S_{11}\Gamma_S)(1 - S_{22}\Gamma_L) - S_{21}S_{12}\Gamma_S\Gamma_L|^2}$$

- In maximizing :
  - Power transfer from the source to the quadripole input  
 $(\Gamma_{in} = S_{11} + S_{12}S_{21}\Gamma_L / (1 - S_{22}\Gamma_L) = \Gamma_S^*)$  « Maximum power gain »
  - Power transfer from the quadripole output to the load  
 $(\Gamma_{out} = S_{22} + S_{12}S_{21}\Gamma_S / (1 - S_{11}\Gamma_S) = \Gamma_L^*)$  « Maximum available gain »

## Maximizing $G_T$ ( $K > 1$ )

- When both input and output are matched (and if it is possible), we have the Maximum Available Gain (MAG)
- $\Gamma_{in} = S_{11} + S_{12}S_{21}\Gamma_L / (1 - S_{22}\Gamma_L) = \Gamma_S^*$
- $\Gamma_{out} = S_{22} + S_{12}S_{21}\Gamma_S / (1 - S_{11}\Gamma_S) = \Gamma_L^*$

$$G_{MAG} = \left| \frac{S_{21}}{S_{12}} \right| \left| K - \sqrt{K^2 - 1} \right| \quad \text{où}$$

$$K = \frac{1 + |\Delta|^2 - |S_{11}|^2 - |S_{22}|^2}{2|S_{12}S_{21}|} > 1$$

$$\Delta = S_{11}S_{22} - S_{12}S_{21}$$

- ↓
- We MUST have  $K > 1$  for MAG adaptation !

## Maximizing $G_T$ ( $K > 1$ )


- $\Gamma_{in} = \Gamma_S^* \Leftrightarrow \Gamma_S = M^* \left( \frac{B_1 \pm \sqrt{B_1^2 - 4|M|^2}}{2|M|^2} \right)$

- $\Gamma_{out} = \Gamma_L^* \Leftrightarrow \Gamma_L = N^* \left( \frac{B_2 \pm \sqrt{B_2^2 - 4|N|^2}}{2|N|^2} \right)$

Use minus sign  
when  $B_1$  is  
positive and  
plus sign when  
 $B_1$  is negative

- $B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2$
- $B_2 = 1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta|^2$
- $M = S_{11} - \Delta S_{22}^*$
- $N = S_{22} - \Delta S_{11}^*$
- $\Delta = S_{11}S_{22} - S_{21}S_{12}$

## Examples

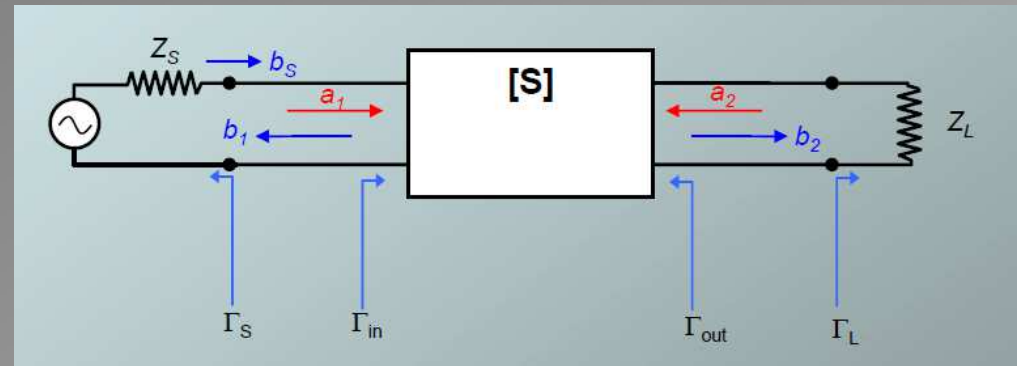

- Let's consider a GaAs MESFET transistor whose S-parameters @ 1GHz are the following :
- $S_{11} = 0.94 \exp -j 45^\circ$        $S_{12} = 0.04 \exp -j 64^\circ$
- $S_{21} = 4.61 \exp j 142^\circ$        $S_{22} = 0.52 \exp -j 20^\circ$
- What is the transducic gain of the transistor when  $Z_S = Z_L = 50\Omega$  ?
- What is the transducic gain of the transistor when  $Z_S = 50\Omega$  and  $Z_L = 100\Omega$  ?
- What is the transducic gain of the transistor when  $Z_S = 100\Omega$  and  $Z_L = 50\Omega$  ?
- What is the transducic gain of the transistor when  $Z_S = Z_L = 100\Omega$  ?
- What is the maximum transducic gain of the transistor when  $Z_S = 50\Omega$  ? What must be the output impedance in this case?
- What is the maximum transducic gain of the transistor when  $Z_L = 50\Omega$  ? What must be the input impedance in this case?
- What is the maximum transducic gain of the transistor?

Ensemble, ré-inventons le monde

$$\begin{aligned}
 S_{11} &= 0.94 \exp -j 45^\circ = 0.665 - j0.665 & S_{12} &= 0.04 \exp -j 64^\circ = 0.0175 - j0.036 \\
 S_{21} &= 4.61 \exp j 142^\circ = -3.63 + j2.84 & S_{22} &= 0.52 \exp -j 20^\circ = 0.49 - j0.18
 \end{aligned}$$

### ANSWERS

- $Z_L = Z_S = 50\Omega$  so  $\Gamma_L = \Gamma_S = 0$  :  $G_T = |S_{21}|^2 = 21.2 = 13.3\text{dB}$
- $Z_S = 50\Omega$  and  $Z_L = 100\Omega$  so  $\Gamma_L = 1/3$  and  $\Gamma_S = 0$  :  $G_T = |S_{21}|^2 (1 - |\Gamma_L|^2) / |1 - S_{22} \Gamma_L|^2 = 21.2 * (8/9) / (0.7036) = 26.8 = 14.3\text{dB}$
- $Z_S = 100\Omega$  and  $Z_L = 50\Omega$  so  $\Gamma_L = 0$  and  $\Gamma_S = 1/3$  :  $G_T = |S_{21}|^2 (1 - |\Gamma_S|^2) / |1 - S_{11} \Gamma_S|^2 = 21.2 * (8/9) / (0.6568) = 28.7 = 14.6\text{dB}$
- $Z_L = Z_S = 100\Omega$  so  $\Gamma_L = \Gamma_S = 1/3$  :
  - $G_T = |S_{21}|^2 (1 - |\Gamma_L|^2) (1 - |\Gamma_S|^2) / |(1 - S_{22} \Gamma_L) (1 - S_{11} \Gamma_S) - S_{21} S_{12} \Gamma_L \Gamma_S|^2$
  - $G_T = 21.2 (8/9)(8/9) / (0.448) = 37.4 = 15.73\text{dB}$
- When  $Z_S = 50\Omega$ ,  $\Gamma_{\text{out}} = S_{22}$ . To achieve the highest gain,  $\Gamma_L$  should be set equal to  $\Gamma_{\text{out}}^* = S_{22}^* = 0.49 + j0.18$  ( $Z_L = 124 + 61.5j\Omega$ )
  - $G_T = G_T = |S_{21}|^2 (1 - |\Gamma_L|^2) / |1 - S_{22} \Gamma_L|^2 = 21.2 * 1.37 = 29.06 = 14.63\text{dB}$
- When  $Z_L = 50\Omega$ ,  $\Gamma_{\text{in}} = S_{11}$ . To achieve the highest gain,  $\Gamma_S$  should be set equal to  $\Gamma_{\text{in}}^* = S_{11}^* = 0.66 + j0.66$  ( $Z_S = 11.7 + 119.7j\Omega$ )
  - $G_T = G_T = |S_{21}|^2 (1 - |\Gamma_S|^2) / |1 - S_{11} \Gamma_S|^2 = 21.2 * 8.59 = 182.1 = 22.6\text{dB}$
- MAG but  $K < 1$  so  $\text{MSG} = |S_{21}/S_{12}| = 115.25 = 20.6\text{dB}$

## Unilaterality

- One common assumption is to assume that the component is unilateral (i.e.  $S_{12} = 0$ )
- In this case :


$$G_T = \frac{|S_{21}|^2 (1 - |\Gamma_S|^2) (1 - |\Gamma_L|^2)}{|(1 - S_{11}\Gamma_S)(1 - S_{22}\Gamma_L) - S_{21}S_{12}\Gamma_S\Gamma_L|^2}$$

$$G_{Tu} = |S_{21}|^2 \frac{1 - |\Gamma_S|^2}{|1 - S_{11}\Gamma_S|^2} \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2}$$

$$G_{Tu}(\text{dB}) = G_0(\text{dB}) + G_S(\text{dB}) + G_L(\text{dB})$$

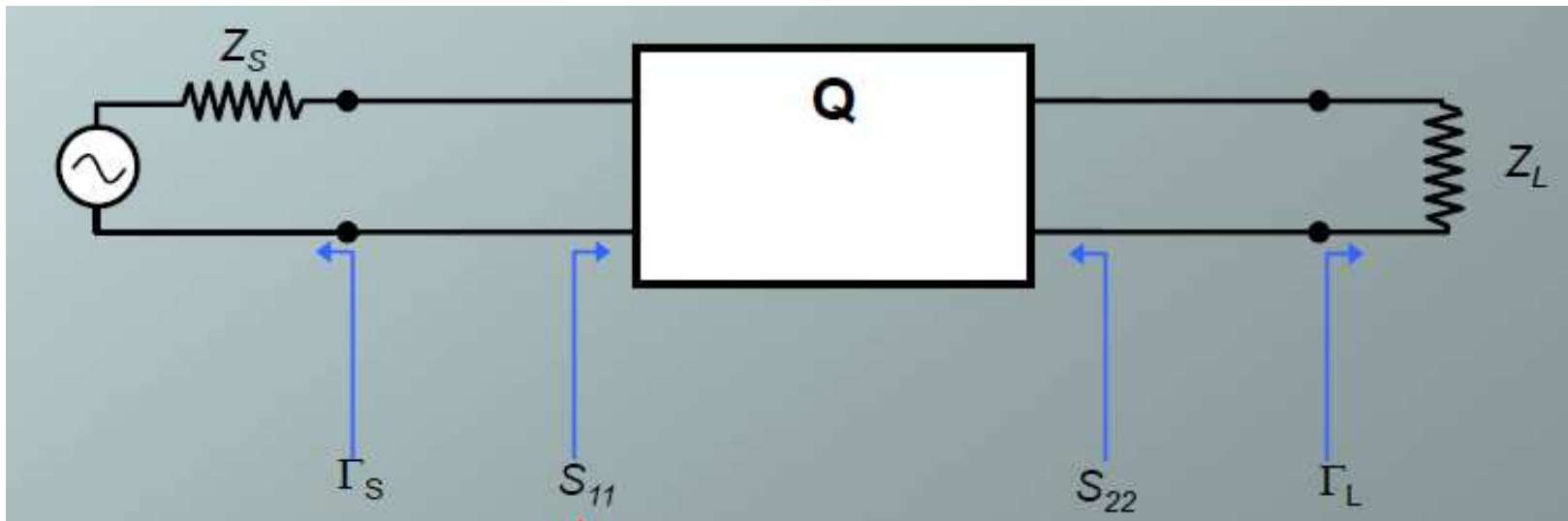
## Unilaterality

- When a component is unilateral :
  - $\Gamma_{in}$  is independent of output load ( $\Gamma_{in} = S_{11}$ )
  - $\Gamma_{out}$  is independent of input load ( $\Gamma_{out} = S_{22}$ )


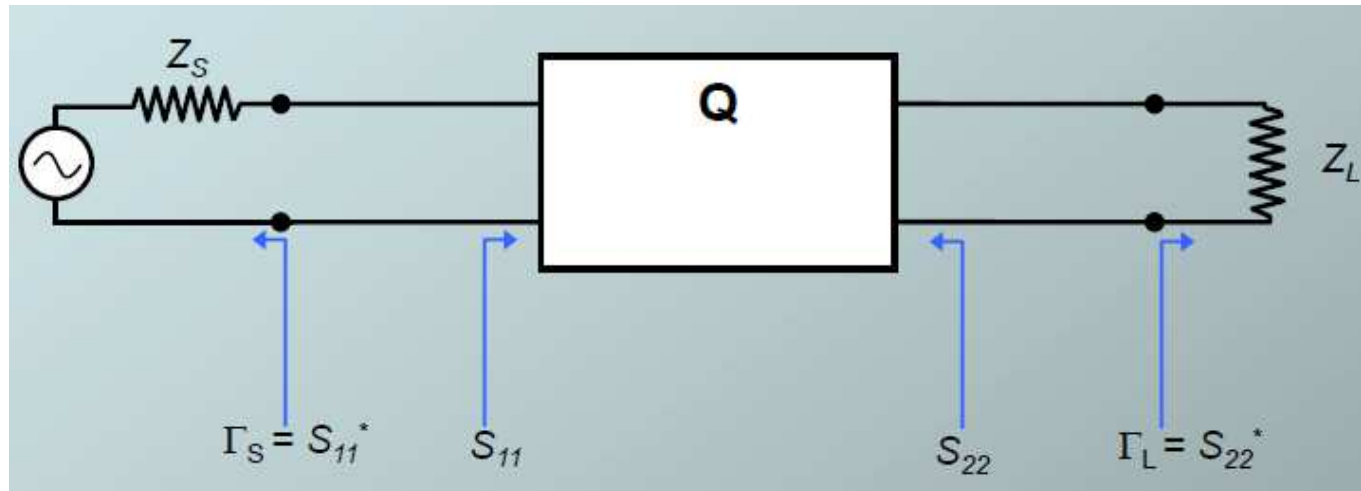
## Maximizing $G_{Tu}$

- To maximize  $G_{Tu}$ , input and output must be matched




$$G_{Tu\max} = |S_{21}|^2 \frac{1}{(1 - |S_{11}|^2)} \frac{1}{(1 - |S_{22}|^2)}$$


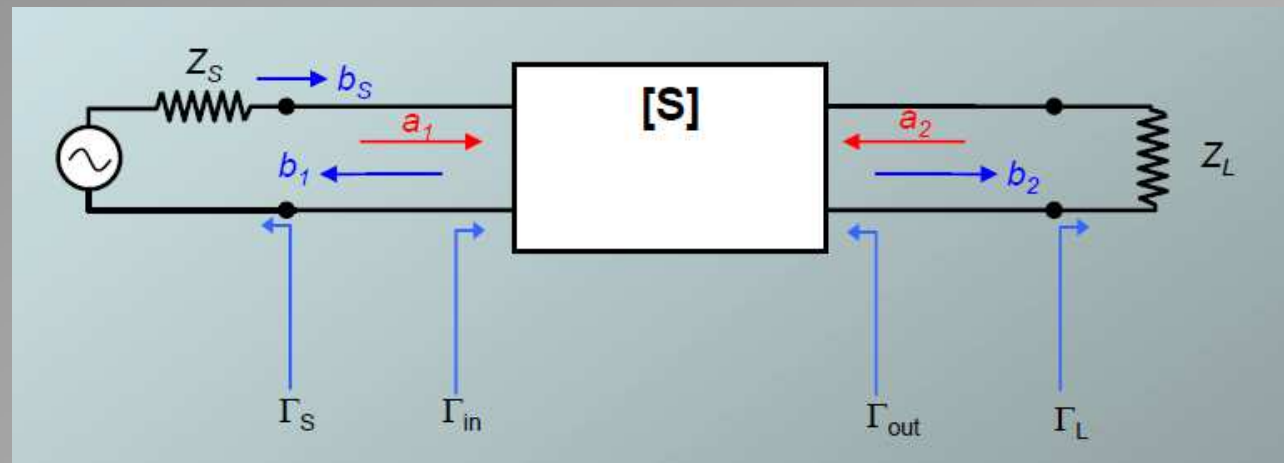
## Example

- Let's consider a GaAs MESFET transistor whose S-parameters @ 1GHz are the following :
- $S_{11} = 0.94 \exp -j 45^\circ$      $S_{12} = 0.04 \exp -j 64^\circ$
- $S_{21} = 4.61 \exp j 142^\circ$      $S_{22} = 0.52 \exp -j 20^\circ$
- What is the maximum unilateral transducic gain?



## Answer

$$G_{Tu\max} = |S_{21}|^2 \frac{1}{(1 - |S_{11}|^2)} \frac{1}{(1 - |S_{22}|^2)}$$

- If the component is supposed to be unilateral,  $G_{Tu} = |4.61|^2 / (1 - 0.94^2)(1 - 0.52)^2 = 250.2 = 24\text{dB}$
- But we have to check the unilaterality assumption !!!

## Unilaterality criterion

$$G_T = \frac{|S_{21}|^2 (1 - |\Gamma_S|^2) (1 - |\Gamma_L|^2)}{|(1 - S_{11}\Gamma_S)(1 - S_{22}\Gamma_L) - S_{21}S_{12}\Gamma_S\Gamma_L|^2}$$

$$G_{Tu} = |S_{21}|^2 \frac{1 - |\Gamma_S|^2}{|1 - S_{11}\Gamma_S|^2} \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2}$$

- When assuming  $S_{12} = 0$ , the  $G_T$  expression turns into the  $G_{Tu}$  expression
- By doing so, you introduce an error (because  $S_{12}$  is never equals to 0), which is :


$$\frac{1}{(1 + u)^2} < \frac{G_T}{G_{Tu}} < \frac{1}{(1 - u)^2}$$

$$u = \frac{|s_{11}s_{22}s_{12}s_{21}|}{|(1 - |s_{11}|^2)(1 - |s_{22}|^2)|}$$

- With
- You have to check whether this error is big or not !!
- 10% error  $\Leftrightarrow u < 0.05$  , 1% error  $\Leftrightarrow u < 0.005$
- $u = 0.1 \Leftrightarrow 20\%$  error,  $u = 0.3 \Leftrightarrow 100\%$  error !
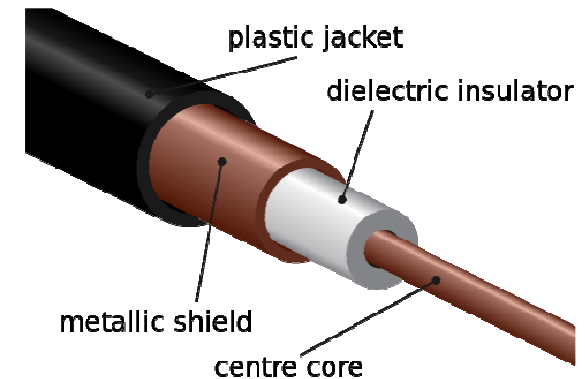
## Example

- Let's consider a GaAs MESFET transistor whose S-parameters @ 1GHz are the following :
- $S_{11} = 0.94 \exp -j 45^\circ$     $S_{12} = 0.04 \exp -j 64^\circ$
- $S_{21} = 4.61 \exp j 142^\circ$     $S_{22} = 0.52 \exp -j 20^\circ$
- Check the unilaterality of the component
- Answer :  $u = 0.94 * 4.61 * 0.04 * 0.52 / (1 - 0.94^2)(1 - 0.52^2)$
- $u = 1.06$
- The device is non-unilateral (we say bilateral), the assumption  $S_{12} = 0$  is wrong !




## Interlude – why 50Ω ?


- Let's consider an air-dielectric coaxial cable
  - $Z_0 = 60/\sqrt{\epsilon_r} \times \ln(\text{outer radius}/\text{inner radius})$
  - Peak electric field =  $E_{\max} = V / ((\text{inner radius}) \times \ln(\text{outer radius}/\text{inner radius}))$
- The max power « capability » of the cable is  $E_{\max}^2/Z_0$ 
  - We find a maximum at the condition : outer radius/inner radius =  $\sqrt{e}$
  - Setting this into  $Z_0$  expression, we find 30Ω
- The attenuation constant in a transmission line is  $R/2Z_0$  where R is the series resistance per unit length
  - $R = (\text{outer radius}^{-1} + \text{inner radius}^{-1}) / (2\pi \times \text{skin depth} \times \text{metal conductivity})$
  - We find a minimum at the condition : outer radius/inner radius = 3.6
  - Setting this into  $Z_0$  expression, we find 77Ω
- An arithmetic or geometric average between these 2 values gives... 50Ω !!
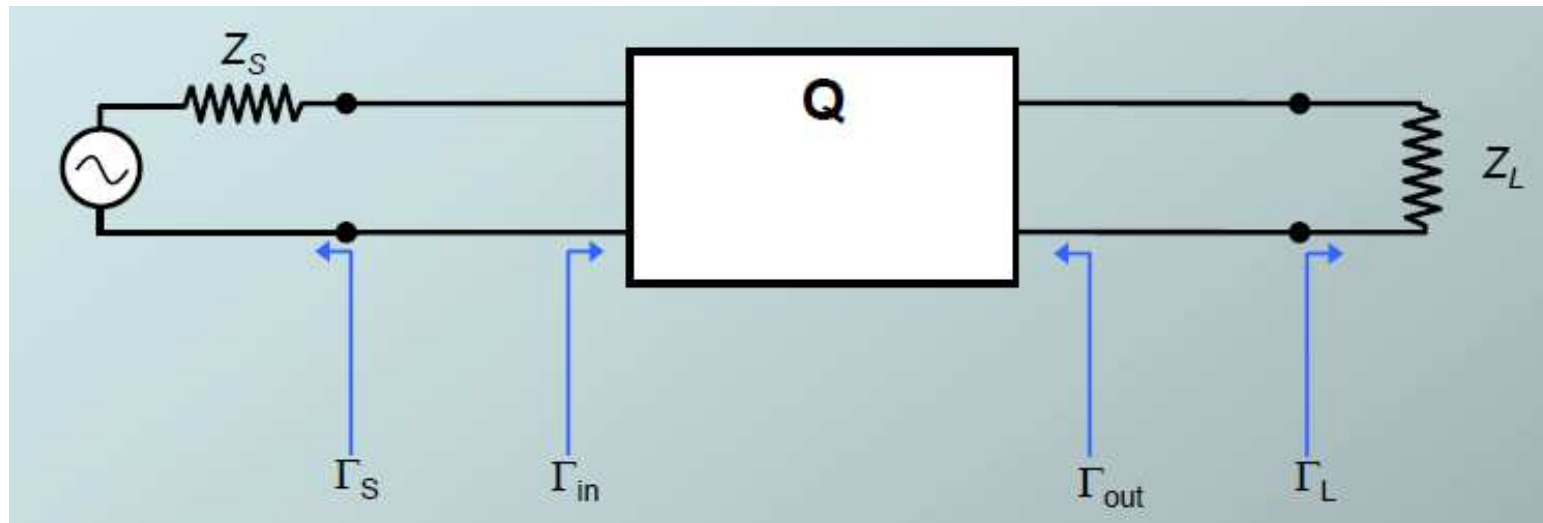
## Stability

- When we want to optimize power transfer, there is a risk that the input wave get reflected at the output and come back to the input : oscillation...
- Unless the component is unilateral !
- instability exists because  $S_{12} \neq 0$




## Stability

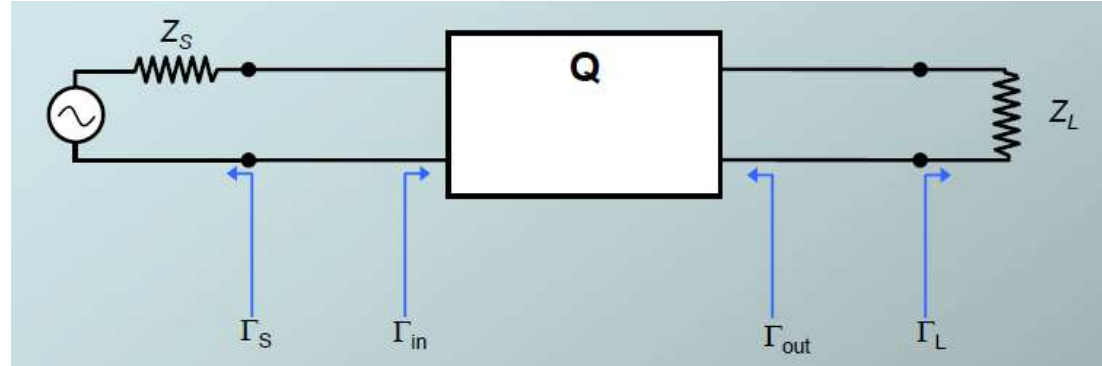

- Instability occurs because energy at one port grows each time a wave is reflected at that port
  - It means that the reflection coefficient has a module higher than 1
- In particular, passive quadripole are always stable
- We have to check the input and output reflection coefficients of the considered component
- $\Gamma_{in} = S_{11} + S_{12} S_{21} \Gamma_L / (1 - S_{22} \Gamma_L)$
- $\Gamma_{out} = S_{22} + S_{21} S_{12} \Gamma_S / (1 - S_{11} \Gamma_S)$
- → Stability depends on input and output loads

## Stability

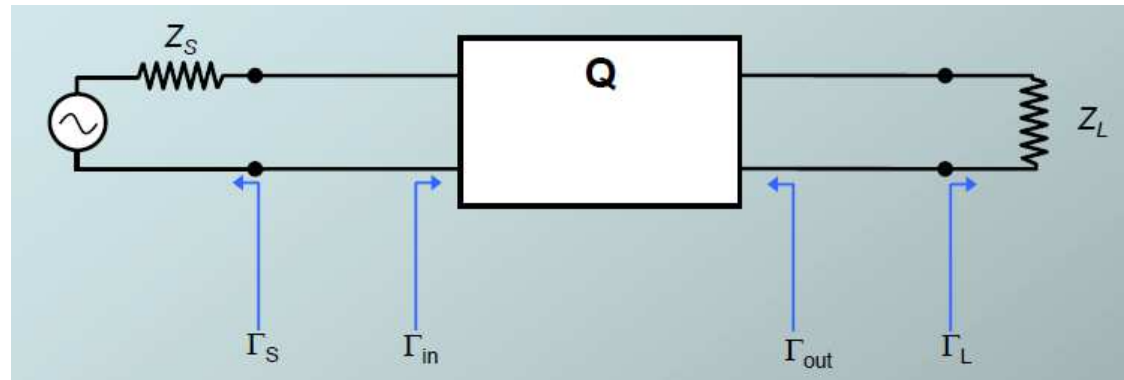

- Stability  $\Leftrightarrow |\Gamma_{in}| < 1$  and  $|\Gamma_{out}| < 1$
- Method : calculate K (Rollett factor):

$$K = \frac{1 + |S_{11}S_{22} - S_{12}S_{21}|^2 - |S_{11}|^2 - |S_{22}|^2}{2|S_{12}S_{21}|}$$

- If  $K > 1$  : the component is unconditionally stable  $\Leftrightarrow$  any loads can be placed both at input and outputs, you can find the MAG
- If  $K < 1$  : the component is potentially unstable  $\Leftrightarrow$  you can not choose any load/source impedance you want  $\rightarrow$  you have to study stability in deeper details




## Stability study

$$|\Gamma_{in}| = |S'_{11}| = \left| S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} \right| < 1$$

$$|\Gamma_{out}| = |S'_{22}| = \left| S_{22} + \frac{S_{12}S_{21}\Gamma_S}{1 - S_{11}\Gamma_S} \right| < 1$$

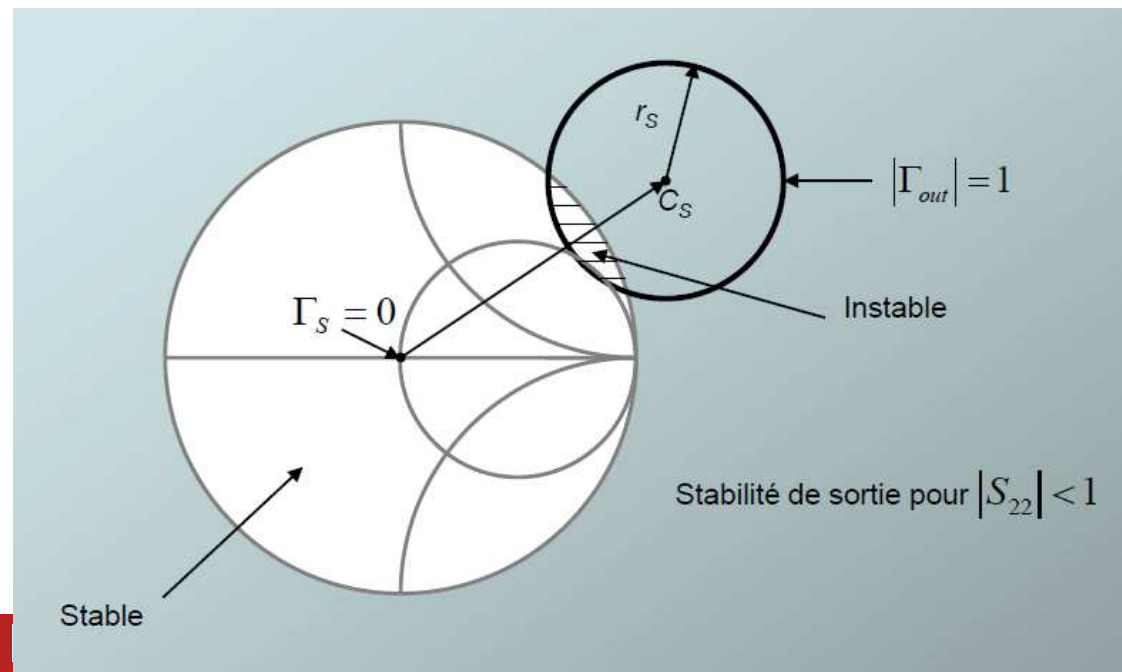- The study of the stability is to find the places of the (im)possible loads in the Smith chart



## Input and output stability circles

$$|\Gamma_{in}| = |S'_{11}| = \left| S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} \right| < 1$$

$$|\Gamma_{out}| = |S'_{22}| = \left| S_{22} + \frac{S_{12}S_{21}\Gamma_S}{1 - S_{11}\Gamma_S} \right| < 1$$

$$r_L = \left| \frac{S_{12}S_{21}}{|S_{22}|^2 - |\Delta|^2} \right|$$

$$c_L = \frac{(S_{22} - \Delta S_{11}^*)^*}{|S_{22}|^2 - |\Delta|^2}$$

$$r_S = \left| \frac{S_{12}S_{21}}{|S_{11}|^2 - |\Delta|^2} \right|$$

$$c_S = \frac{(S_{11} - \Delta S_{22}^*)^*}{|S_{11}|^2 - |\Delta|^2}$$


$$\Delta = S_{11}S_{22} - S_{21}S_{12}$$

## Example

- Let's consider a GaAs MESFET transistor whose S-parameters @ 1GHz are the following :
- $S_{11} = 0.94 \exp -j 45^\circ$      $S_{12} = 0.04 \exp -j 64^\circ$
- $S_{21} = 4.61 \exp j 142^\circ$      $S_{22} = 0.52 \exp -j 20^\circ$
- Is this transistor stable @ 1GHz?
- If unstable, draw the input and output stability circles

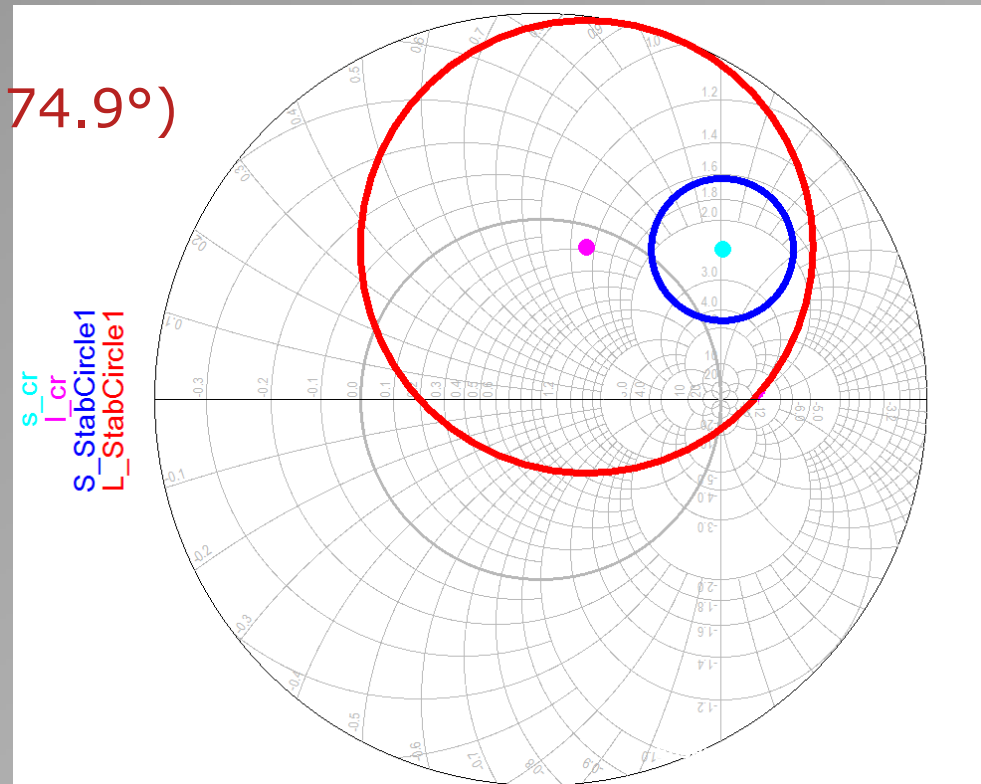
## Answers

- $K = 0.2629 / 0.3688 = 0.7129$
- $< 1$  conditionally stable
- $\Delta = 0.17 - j0.62 = 0.65 \exp(-j74.9^\circ)$
- $r_L = 1.26$
- $c_L = 0.89 \exp(j73.2^\circ)$
- $r_S = 0.39$
- $c_S = 1.31 \exp(j39.6^\circ)$


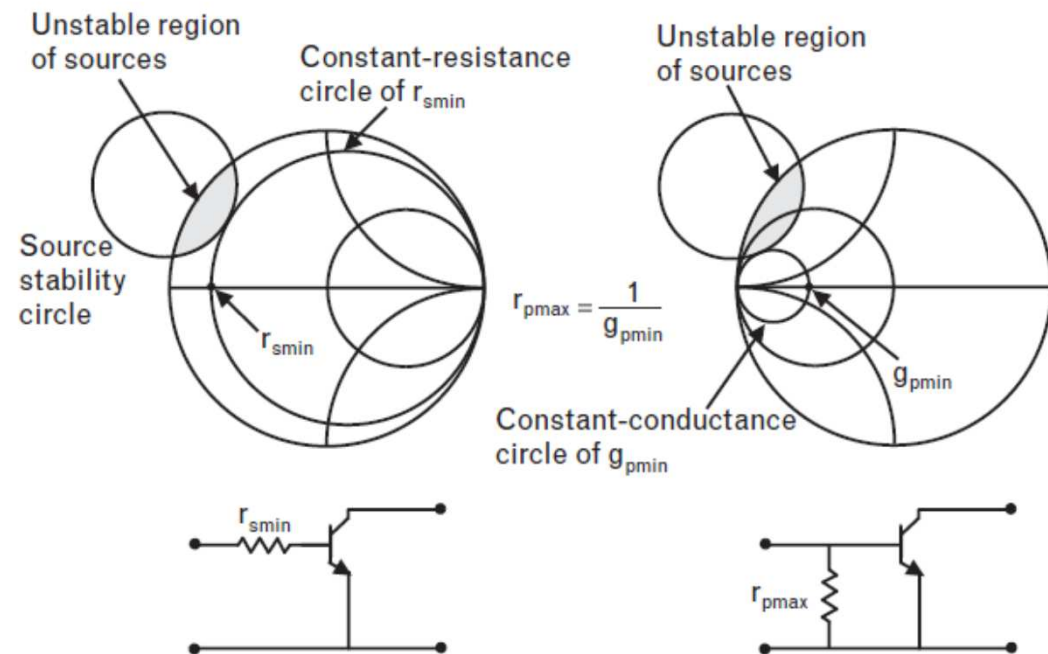
## How to stabilize an unstable component

- Many ways to do it...
- The easiest (but not the most performant...) consists in introducing a lossy element (in series or in parallel) at the input and/or the output of the component
- This element will dissipate energy and will stabilize the component
  - Less gain
  - More noise
- To calculate the value :





## Example

- Let's consider a GaAs MESFET transistor whose S-parameters @ 1GHz are the following :
- $S_{11} = 0.94 \exp -j 45^\circ$        $S_{12} = 0.04 \exp -j 64^\circ$
- $S_{21} = 4.61 \exp j 142^\circ$        $S_{22} = 0.52 \exp -j 20^\circ$
- Calculate the series resistor (inserted at the input) used to stabilize the component @ 1GHz
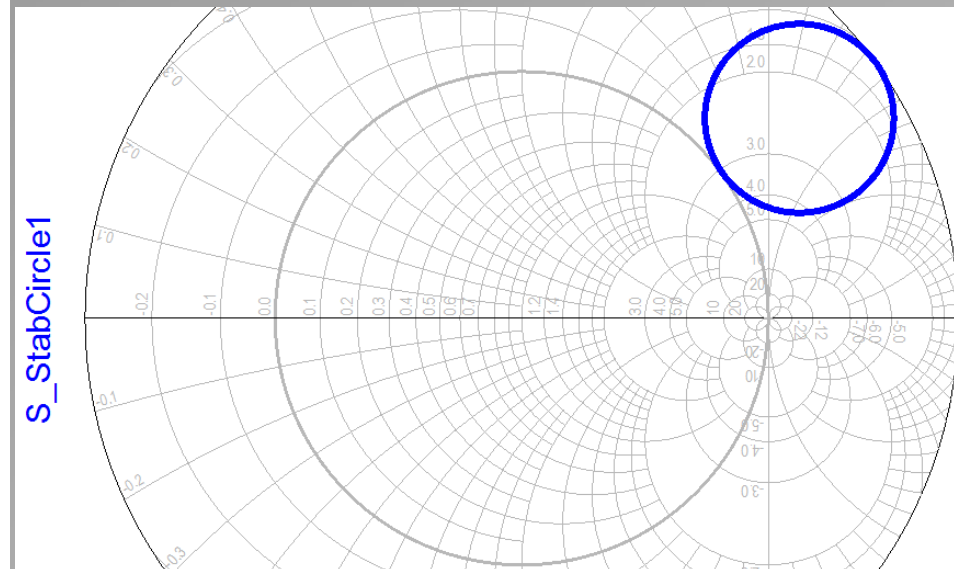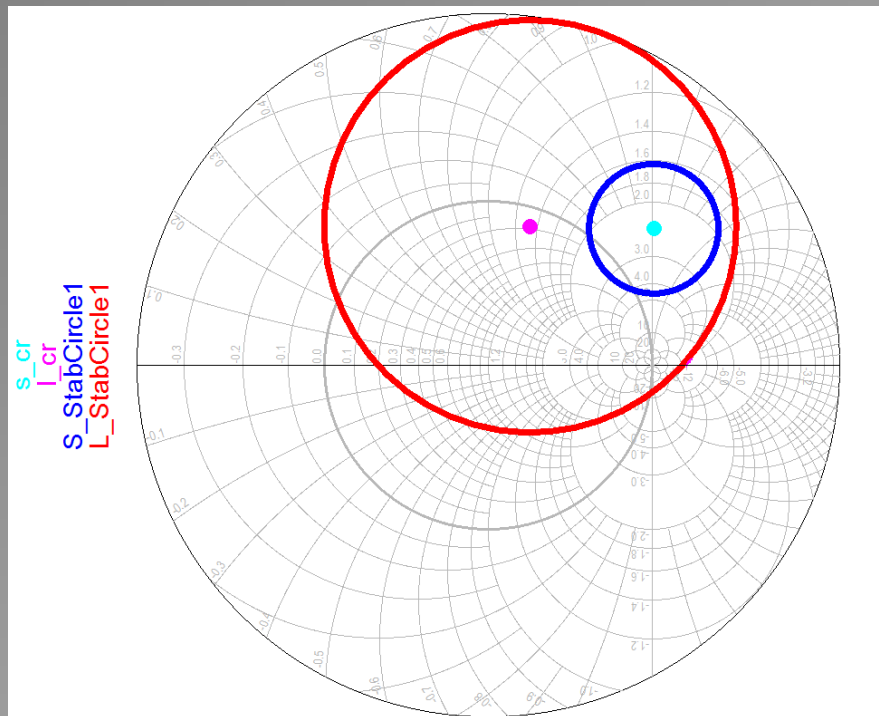
## Answers

- $r_{\min} = 0,4$
- $R_{\min} = 0,4 * 50 = 20 \text{ Ohms}$



$$\begin{cases} V_1 = AV_2 - BI_2 \\ I_1 = CV_2 - DI_2 \end{cases}$$

## BUT...

- Introducing a resistor in series or in parallel modifies the S-parameters of the overall component...
- Gain calculation should be done with this new configuration of parameters
- Unfortunately, S parameters matrices can not be multiplied...
  - Go into ABCD form for the extra resistor and the component
  - Multiply the matrices
  - Go back into S-parameters form... !

$$A = \frac{(1 + S_{11})(1 - S_{22}) + S_{12}S_{21}}{2S_{21}} \quad S_{11} = \frac{A + B - C - D}{A + B + C + D}$$

$$B = \frac{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}{2S_{21}} \quad S_{12} = \frac{2\Delta_c}{A + B + C + D}$$

$$C = \frac{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}{2S_{21}} \quad S_{21} = \frac{2}{A + B + C + D}$$

$$D = \frac{(1 - S_{11})(1 + S_{22}) + S_{12}S_{21}}{2S_{21}} \quad S_{22} = \frac{-A + B - C + D}{A + B + C + D}$$



## New S-parameters matrix

- In particular, the new S-parameters matrix is (for a series resistance at the input) :
- New S =

$$\frac{1}{1 + \frac{r}{2}(1 - S_{11})} \begin{pmatrix} S_{11} + \frac{r}{2}(1 - S_{11}) & S_{12} \\ S_{21} & S_{22} + \frac{r}{2}(S_{22} - S_{11}S_{22} + S_{12}S_{21}) \end{pmatrix}$$

## EXAMPLE

- Let's consider a GaAs MESFET transistor whose S-parameters @ 1GHz are the following :
- $S_{11} = 0.94 \exp -j 45^\circ$        $S_{12} = 0.04 \exp -j 64^\circ$
- $S_{21} = 4.61 \exp j 142^\circ$        $S_{22} = 0.52 \exp -j 20^\circ$
- Find the new S-parameters including the extra resistor of 22 Ohms (+10% safety margin)
- What is the MAG?

## Answers

- $S_{11} = 0.94 \exp -j 45^\circ$
- $S_{21} = 4.61 \exp j 142^\circ$
- $S_{12} = 0.04 \exp -j 64^\circ$
- $S_{22} = 0.52 \exp -j 20^\circ$
- $S_{11} = 0.84 \exp -j 43^\circ$
- $S_{21} = 4.28 \exp j 135^\circ$
- $S_{12} = 0.037 \exp -j 71^\circ$
- $S_{22} = 0.52 \exp -j 16^\circ$
- $K = 1,015$
- $MAG = 4,28/0,04 * (1,015 - \sqrt{1,015^2 - 1}) = 107 * 0,841 = 90 = 19,6dB$


## Noise

- Noise Factor : N or F
- Shows the degradation of the SNR between the input and the output of the component

$$F = \frac{(Signal / noise)_{input}}{(Signal / noise)_{output}}$$

- To fully characterize a noisy component : 3 parameters :
  - $F_{min}$  : Minimum Noise factor of the quadripole
  - $\Gamma_{opt}$  (or  $Z_{opt}$ ) : the reflection coefficient leading to  $F_{min}$
  - $R_n$  : Equivalent noise resistance (shows how fast noise factor increases as we move away from  $\Gamma_{opt}$ )

## Noise

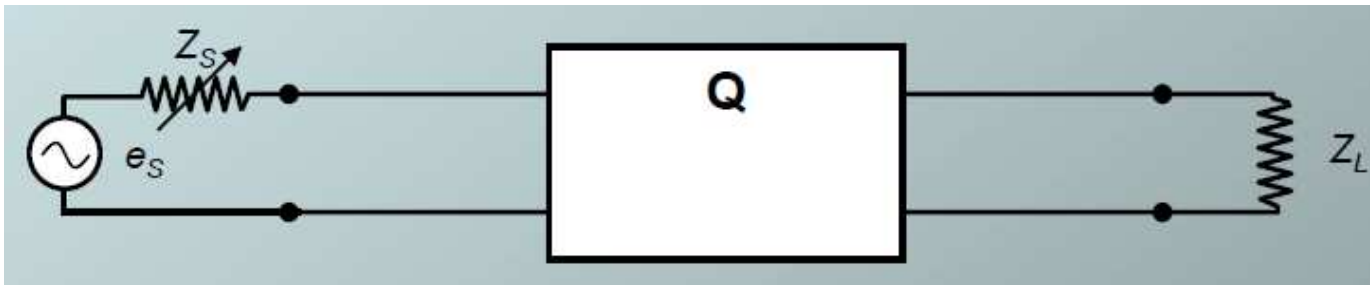

$$F = F_{\min} + 4R_n \frac{|\Gamma_s - \Gamma_{opt}|^2}{(1 - |\Gamma_s|^2)(1 + |\Gamma_{opt}|^2)}$$

**F only depends on  $Z_s$  !**


## Noise

- $F = \text{cst}$  : give circles in Smith chart

$$N_i = \frac{F_i - F_{MIN}}{4r_n} |1 + \Gamma_{opt}|^2 = \frac{|\Gamma_S - \Gamma_{opt}|^2}{1 - |\Gamma_S|^2}$$

$$r_{Fi} = \frac{1}{1 + N_i} \sqrt{N_i^2 + N_i (1 - |\Gamma_{opt}|^2)}$$
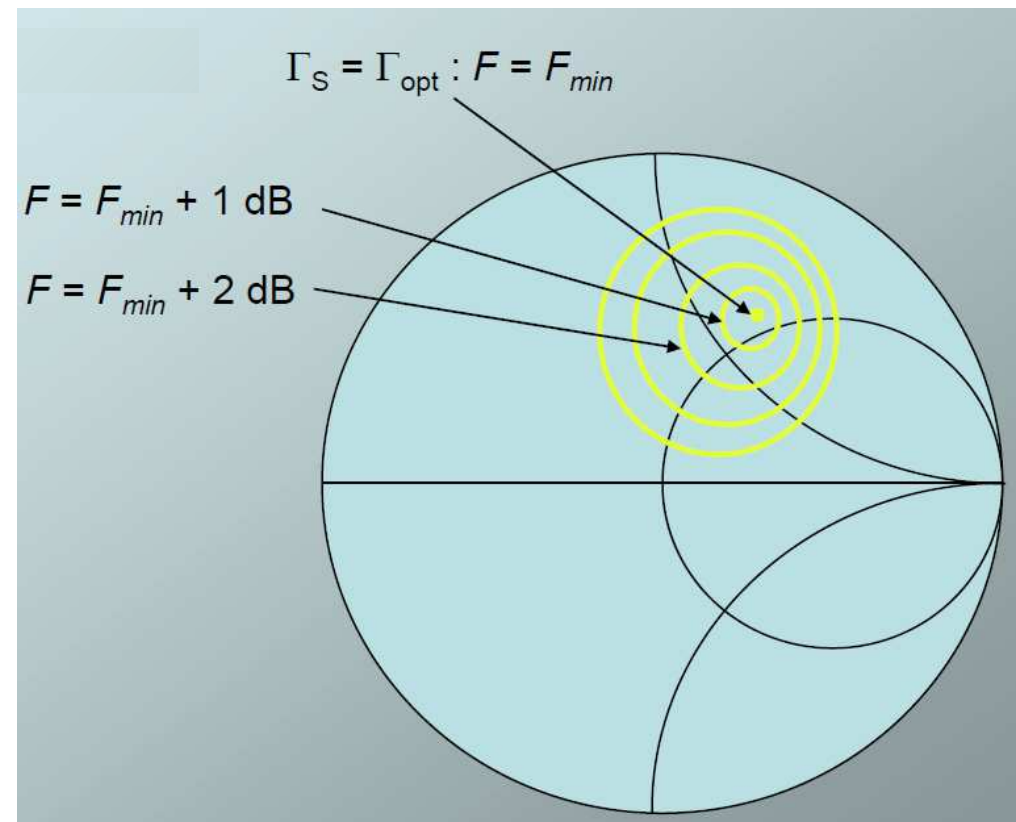
$$c_{Fi} = \frac{\Gamma_{opt}}{1 + N_i}$$



## Example

- $F_{\min} = 0.66 \text{ dB}$
- $\Gamma_{\text{opt}} = 0.47 \exp(j30^\circ)$
- $R_n = 12\Omega$
- Draw the 1dB noise circle

## Answer


- $F_{\min} = 0.66\text{dB} = 1.164$
- $F = 1\text{dB} = 1.26$
- $r_N = R_N/50 = 0.24$

- $N_{1\text{dB}} = (1.26 - 1.164) / (4 \times 0.24) \times \text{abs}(1 + 0.407 + j0.235)^2$   
 $= 0.1 \times 2.035 = 0.203$
- $r_{F1\text{dB}} = (1/1.203) \times \text{sqrt}(0.203^2 + 0.203(1 - 0.47^2)) = 0.371$
- $c_{F1\text{dB}} = 0.39 \exp(j30^\circ)$

$$N_i = \frac{F_i - F_{\min}}{4r_n} |1 + \Gamma_{\text{opt}}|^2 = \frac{|\Gamma_S - \Gamma_{\text{opt}}|^2}{1 - |\Gamma_S|^2}$$

$$r_{Fi} = \frac{1}{1 + N_i} \sqrt{N_i^2 + N_i(1 - |\Gamma_{\text{opt}}|^2)}$$
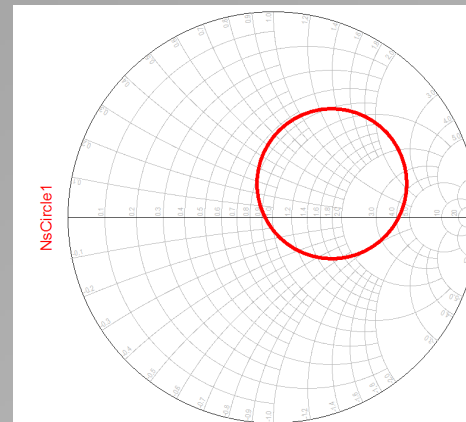
$$c_{Fi} = \frac{\Gamma_{\text{opt}}}{1 + N_i}$$





## Methodology of design

- Stability factor calculation
    - OK → all the impedances with a positive real part are possible
    - Not OK : draw the circles and check the possible source and load impedances
    - Stabilize the component with dissipative components (Resistors)
    - Calculate the new S-parameters
  - Unilateral factor calculation
    - OK : unilateral design
    - Not OK : bilateral design
  - Choose a desirable NF (if required) and draw the circle
- Noise-oriented design :
- Once  $\Gamma_S$  is fixed, calculate  $\Gamma_{out} = S_{22} + S_{21}S_{12}\Gamma_S / (1 - S_{11}\Gamma_S)$
  - Choose  $\Gamma_L = \Gamma_{out}^*$  for maximum power transfer
- 
- $\Gamma_S$  and  $\Gamma_L$  are now fixed, let's see how we build them !
  - Next lesson : impedance adaptation networks